

Lab 9-10 Nanoprocessor Design Competition
CS1050 Computer Organization and Digital Design

Group number – 14

Members:


<i>Name</i>	<i>Index number</i>
Illangasinghe I.M.D.P	220234R
Dissanayake D.M.S.H	220138C
Balasuriya B.D.S.K	220056X
Fernando K.M.I	220166J

Lab Task

- Designing and developing a 4-bit arithmetic unit capable of completing addition and subtraction on signed integers.
- Designing and developing instruction decoder to decode 12 bit instructions and activate necessary components in the processor accordingly.
- Designing and developing other required components to create the processor.
 - Register Bank
 - Program Rom
 - Program Counter
 - Multiplexers (Using Tri-state Buffers)
 - 3-bit adder
 - Slow clock
- Verifying the processor functionality via Xilinx Vivado simulation.
- Testing the processor in Basys 3 FPGA board.

Design Diagrams and Simulation

- Lookup table for Seven segment display

 

```
-- Module Name: LUT_16_7 - Behavioral

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use ieee.numeric_std.all;

-- seven segment LUT
entity LUT_16_7 is
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));
end LUT_16_7;

architecture Behavioral of LUT_16_7 is

    type rom_type is array (0 to 15) of std_logic_vector(6 downto 0);

    signal sevenSegment_ROM : rom_type := (
        "1000000", -- 0
        "1111001", -- 1
        "0100100", -- 2
        "0110000", -- 3
        "0011001", -- 4
        "0010010", -- 5
        "0000010", -- 6
        "1111000", -- 7
        "0000000", -- 8
        "0010000", -- 9
        "0001000", -- a
        "0000011", -- b
        "1000110", -- c
        "0100001", -- d
        "0000110", -- e
        "0001110"  -- f
    );

begin
    data <= sevenSegment_ROM(to_integer(unsigned(address)));
end Behavioral
```

- Unit testing and Simulation

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_SevenSeg is
-- Port ( );
end TB_SevenSeg;

architecture Behavioral of TB_SevenSeg is

component LUT_16_7 is
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));
end component;

signal address : STD_LOGIC_VECTOR (3 downto 0);
signal data : STD_LOGIC_VECTOR (6 downto 0);

begin
UUT:LUT_16_7 port map(address,data);

process begin

    address<="0000";
    wait for 50 ns;
    address<="0001";
    wait for 50 ns;
    address<="0010";
    wait for 50 ns;
    address<="0011";
    wait for 50 ns;
    address<="0100";
    wait for 50 ns;
    address<="0101";
    wait for 50 ns;
    address<="0110";
    wait for 50 ns;
    address<="0111";
    wait for 50 ns;
    address<="1000";
    wait for 50 ns;
    address<="1001";
    wait for 50 ns;
    address<="1010";
    wait for 50 ns;
    address<="1011";
    wait for 50 ns;
    address<="1100";
    wait for 50 ns;
    address<="1101";
    wait for 50 ns;
    address<="1110";
    wait for 50 ns;
    address<="1111";
    wait for 50 ns;
    address<="1110";
```

```


        wait;
    end process;

    end Behavioral;

```

Name	Value	0 ns100 ns200 ns300 ns400 ns500 ns600 ns700 ns															
> address[3:0]	1110	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011	1100	1101	1110	1111
> data[6:0]	0000110	1000	1111	0100	0110	0011	0010	0000	1111	0000	0010	0001	0000	1000	0100	0000	0001

- Slow Clock

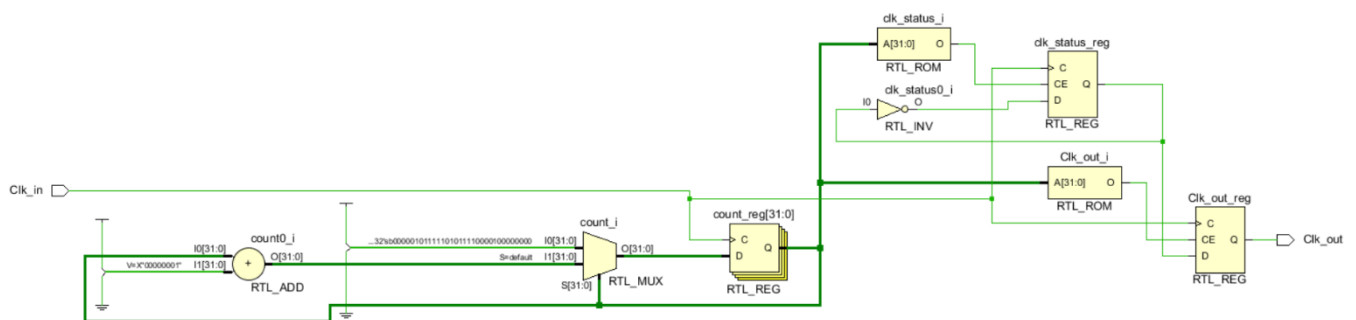

```
-- Module Name: Slow_Clk - Behavioral
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
           Clk_out : out STD_LOGIC);
end Slow_Clk;

architecture Behavioral of Slow_Clk is

    signal count:integer := 1;
    signal clk_status : std_logic := '0';

begin
    process (Clk_in)
    begin
        if rising_edge(Clk_in) then
            count <= count + 1;
            if (count = 100000000) then

```

```

        clk_status <= not clk_status;
        Clk_out <= clk_status;
        count <= 1;
    end if;
end if;
end process;

end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_slowclock is
-- Port ( );
end TB_slowclock;

architecture Behavioral of TB_slowclock is
    component Slow_Clk is
        Port ( Clk_in : in STD_LOGIC;
              Clk_out : out STD_LOGIC);
    end component;
    signal Clk_in : STD_LOGIC;
    signal Clk_out : STD_LOGIC;


begin

    UUT:Slow_Clk port map(Clk_in,Clk_out);


    process begin
        Clk_in<='1';
        wait for 5 ns;
        Clk_in<='0';
        wait for 5 ns;
    end process;

end Behavioral;

```

 

- Half adder

 

```
-- Module Name: HA - Behavioral

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Half adder;
entity HA is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           S : out STD_LOGIC;
           C : out STD_LOGIC);
end HA;

architecture Behavioral of HA is

begin
    S<=A XOR B;
    C<=A AND B;

end Behavioral;
```

- Unit testing and Simulation

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_HA is
    -- Port ( );
end TB_HA;

architecture Behavioral of TB_HA is
    COMPONENT HA
        PORT(A,B :IN STD_LOGIC;
             S,C:OUT STD_LOGIC);
    END COMPONENT;

    SIGNAL a,b: std_logic;
    SIGNAL s,c : std_logic;
```

```


begin

UUT: HA PORT MAP (
    A=>a,
    B=>b,
    S=>s,
    C=>c
);


process
begin
    a<='0';
    b<='0';
    WAIT FOR 100 ns;
    b<='1';
    WAIT FOR 100 ns;
    a<='1';
    b<='0';
    WAIT FOR 100 ns;
    b<='1';
    WAIT;
end process;

end Behavioral;

```

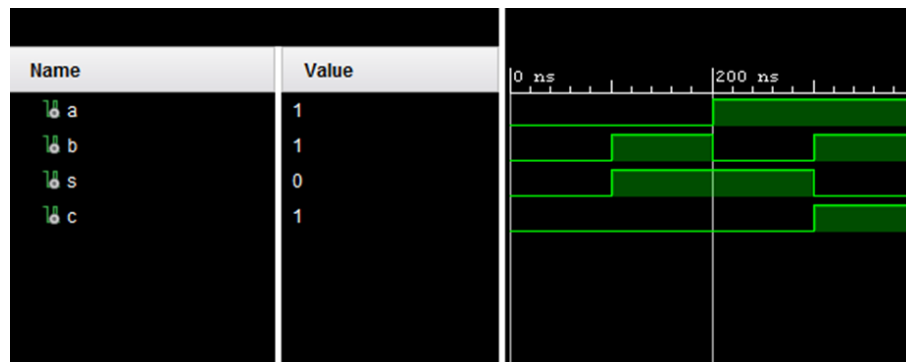

- Full adder

 

-- Module Name: FA - Behavioral

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Full Adder

entity FA is

Port (

A : in STD_LOGIC;

B : in STD_LOGIC;

C_in : in STD_LOGIC;

S : out STD_LOGIC;

C_out : out STD_LOGIC

);

end FA;

architecture Behavioral of FA is

COMPONENT HA

PORT (

A : IN STD_LOGIC;

B : IN STD_LOGIC;

S : OUT STD_LOGIC;

C : OUT STD_LOGIC

);

END COMPONENT;

SIGNAL HA0_S, HA0_C, HA1_S, HA1_C : STD_LOGIC;

begin

HA_0 : HA port map (

A => A,

B => B,

S => HA0_S,

C => HA0_C

);

HA_1 : HA port map (

A => HA0_S,

B => C_in,

S => HA1_S,


```

        C => HA1_C
    );

    S <= HA1_S;
    C_out <= HA1_C OR HA0_C;
end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_FA is
    -- Port ( );
end TB_FA;

architecture Behavioral of TB_FA is
    COMPONENT FA
        PORT(A,B,C_in :IN STD_LOGIC;
             S,C_out:OUT STD_LOGIC);
    END COMPONENT;

    SIGNAL a,b,c_in: std_logic;
    SIGNAL s,c_out  : std_logic;
begin

    UUT: FA PORT MAP(
        A=>a,
        B=>b,
        C_in=>c_in,
        S=>s,
        C_out=>c_out
    );

    process
    begin
        a<='0';
        b<='0';
        c_in<='0';
        WAIT FOR 100 ns;
        c_in<='1';
        WAIT FOR 100 ns;
        b<='1';
        c_in<='0';
        WAIT FOR 100 ns;
        c_in<='1';
        WAIT FOR 100 ns;
        a<='1';
        b<='0';
        c_in<='0';
        WAIT FOR 100 ns;
        c_in<='1';
        WAIT FOR 100 ns;
        b<='1';
        c_in<='0';
    end process


```

```


        WAIT FOR 100 ns;
        c_in<='1';
        WAIT;
    end process;

end Behavioral;

```

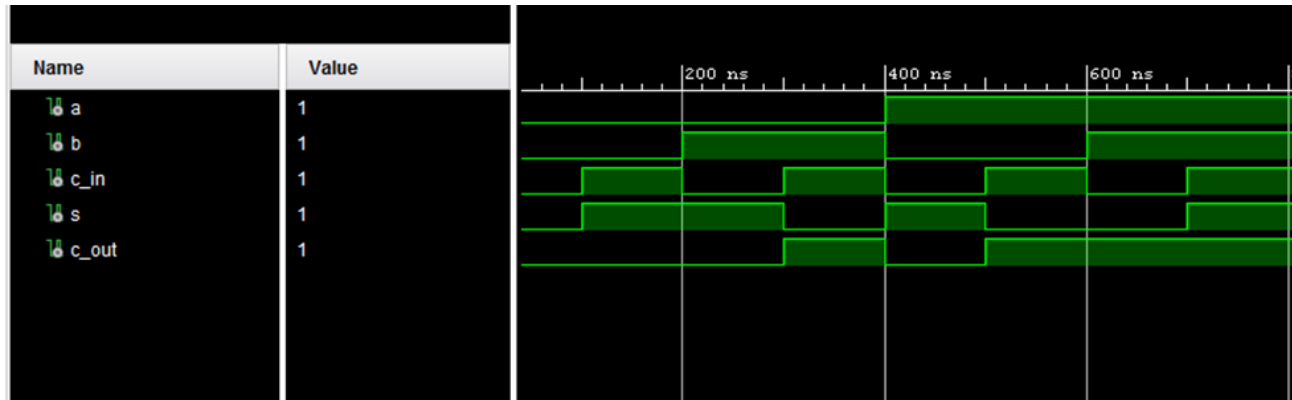

- Comparator

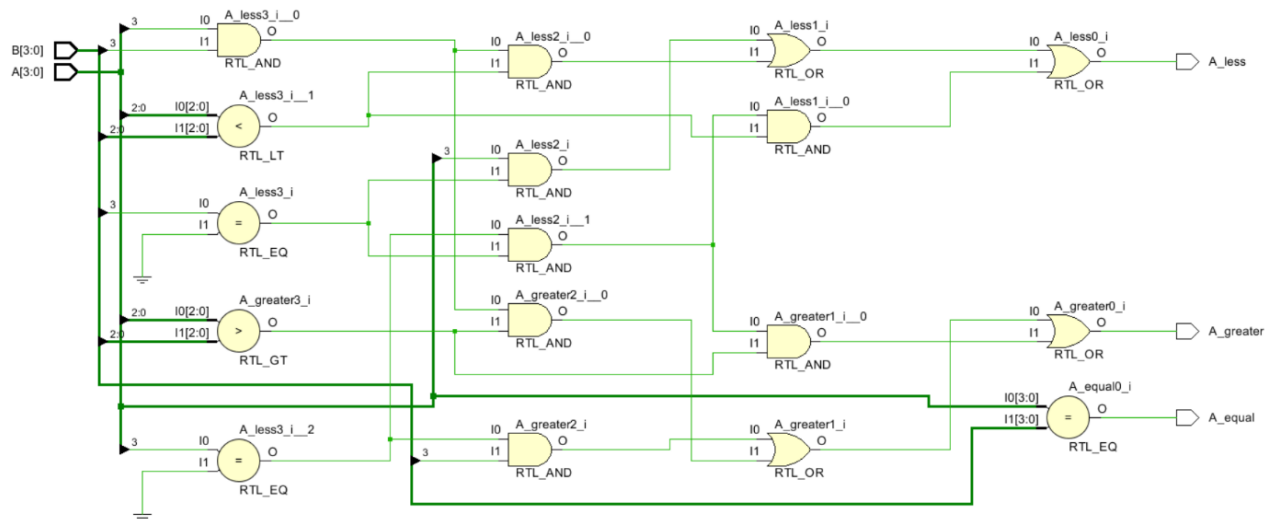

-- Module Name: comparator - Behavioral

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

-- comparator for comparison of two values selected by Data Bus

```

entity comparator is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);

```

```

        A_less : out STD_LOGIC;
        A_equal : out STD_LOGIC;
        A_greater : out STD_LOGIC);
end comparator;

architecture Behavioral of comparator is

    signal vA_equal:std_logic_vector (3 downto 0);
    signal vA_less: std_logic;

begin

    vA_less <= '1' when (A(3)='1' and B(3)='0') else '0';

    A_less <='1' when (vA_less='1' or (A(3)='1' and B(3)='1' and A(2 downto 0)<B(2 downto 0)) or (A(3)='0' and B(3)='0' and A(2 downto 0)<B(2 downto 0))) else '0';

    A_equal <='1' when (A=B) else '0';

    A_greater <='1' when ((A(3)='0' and B(3)='1') or (A(3)='1' and B(3)='1' and A(2 downto 0)>B(2 downto 0)) or (A(3)='0' and B(3)='0' and A(2 downto 0)>B(2 downto 0))) else '0';

end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_FA is
    -- Port ( );
end TB_FA;

architecture Behavioral of TB_FA is
    COMPONENT FA
        PORT(A,B,C_in :IN STD_LOGIC;
             S,C_out:OUT STD_LOGIC);
    END COMPONENT;

    SIGNAL a,b,c_in: std_logic;
    SIGNAL s,c_out : std_logic;
begin

    UUT: FA PORT MAP(
        A=>a,
        B=>b,
        C_in=>c_in,
        S=>s,
        C_out=>c_out
    );

    process
    begin
        a<='0';


```

```


b<='0';
c_in<='0';
WAIT FOR 100 ns;
c_in<='1';
WAIT FOR 100 ns;
b<='1';
c_in<='0';
WAIT FOR 100 ns;
c_in<='1';
WAIT FOR 100 ns;
a<='1';
b<='0';
c_in<='0';
WAIT FOR 100 ns;
c_in<='1';
WAIT FOR 100 ns;
b<='1';
c_in<='0';
WAIT FOR 100 ns;
c_in<='1';
WAIT;
end process;

```

end Behavioral;

 

-ALU

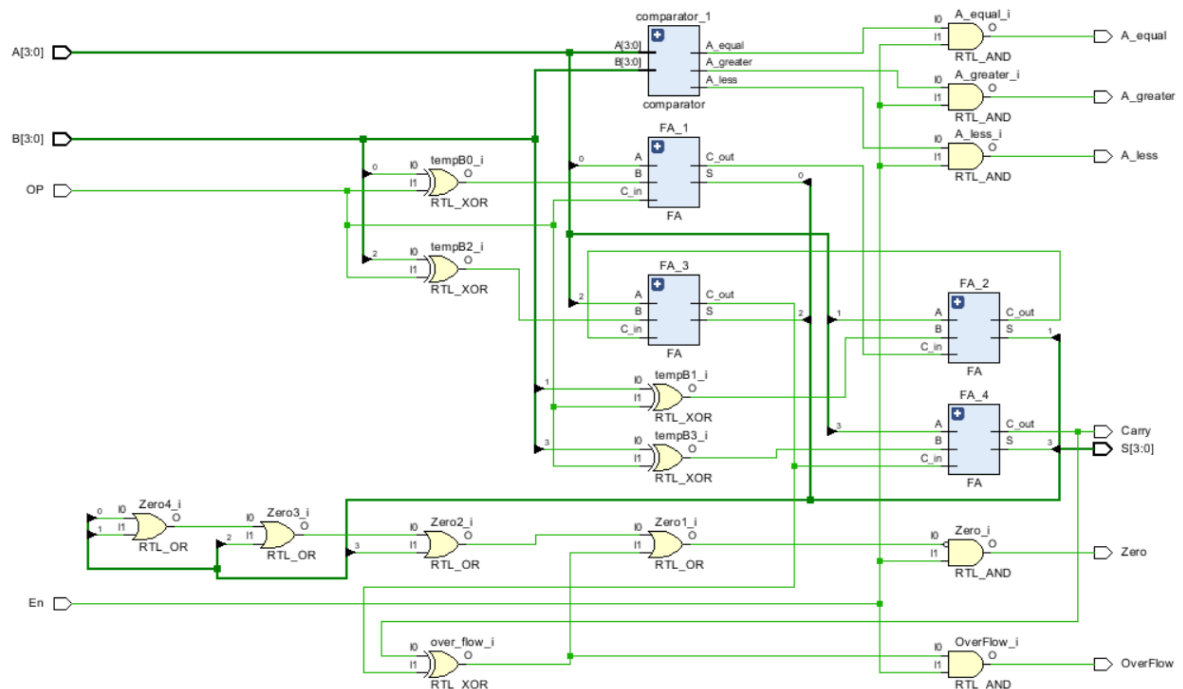

-- Module Name: RCA_4 - Behavioral

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RCA_4 is
    Port (
        A: in STD_LOGIC_VECTOR (3 downto 0) ;
        B: in STD_LOGIC_VECTOR (3 downto 0);
        OP, En : in STD_LOGIC;
        S : out STD_LOGIC_VECTOR (3 downto 0);
        OverFlow, Zero, Carry, A_less, A_equal, A_greater : out STD_LOGIC);
end RCA_4;
```

```
architecture Behavioral of RCA_4 is
    component comparator is
        Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
              B : in STD_LOGIC_VECTOR (3 downto 0);
              A_less : out STD_LOGIC;
              A_equal : out STD_LOGIC;
              A_greater : out STD_LOGIC);
    end component;
```

```
    component FA
        port (
            A: in std_logic;
            B: in std_logic;
            C_in: in std_logic;
```

```

S: out std_logic;
C_out: out std_logic);
end component;

SIGNAL vA_less,vA_equal,vA_greater,over_flow,FA0_S, FA0_C, FA1_S, FA1_C,
FA2_S, FA2_C, FA3_S, FA3_C,tempB0,tempB1,tempB2,tempB3,cout : std_logic;
signal S_temp : std_logic_vector (3 downto 0);

begin

    comparator_1:comparator port map(A,B,vA_less,vA_equal,vA_greater);

    A_less<=vA_less and En;
    A_equal<=vA_equal and En;
    A_greater<=vA_greater and En;
    tempB0<=B(0) XOR OP;
    tempB1<=B(1) XOR OP;
    tempB2<=B(2) XOR OP;
    tempB3<=B(3) XOR OP;

    FA_1 : FA
    port map (
        A => A(0),
        B =>tempB0,
        C_in => OP, -- Set to ground
        S => S_temp(0),
        C_Out => FA0_C);

    FA_2 : FA
    port map (
        A => A(1),
        B => tempB1,
        C_in => FA0_C,
        S => S_temp(1),
        C_Out => FA1_C);

    FA_3 : FA
    port map (
        A => A(2),
        B =>tempB2,
        C_in => FA1_C,
        S => S_temp(2),
        C_Out => FA2_C);

    FA_4 : FA
    port map (
        A => A(3),
        B => tempB3,
        C_in => FA2_C,
        S => S_temp(3),
        C_Out => cout);

    S<=S_temp;
    over_flow <= cout XOR FA2_c;
    Carry <= cout;
    Zero <= not (S_temp(0) or S_temp(1) or S_temp(2) or S_temp(3) or
over_flow) and En;

```

```

    OverFlow <= over_flow and En;

end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_ALU is
-- Port ( );
end TB_ALU;

architecture Behavioral of TB_ALU is
component RCA_4 is
    Port (
        A: in STD_LOGIC_VECTOR (3 downto 0) ;
        B: in STD_LOGIC_VECTOR (3 downto 0);
        OP,En : in STD_LOGIC;
        S : out STD_LOGIC_VECTOR (3 downto 0);
        OverFlow,Zero,Carry,A_less,A_equal,A_greater : out STD_LOGIC);
end component;
signal A : STD_LOGIC_VECTOR (3 downto 0) ;
signal B : STD_LOGIC_VECTOR (3 downto 0);
signal OP,En : STD_LOGIC;
signal S : STD_LOGIC_VECTOR (3 downto 0);
signal OverFlow,Zero,Carry,A_less,A_equal,A_greater : STD_LOGIC;

begin

UUT:RCA_4 port map(A,B,OP,En,S,
OverFlow,Zero,Carry,A_less,A_equal,A_greater);
process begin
    En<='1';
    A<="0001";
    B<="0010";
    OP<='0';

    wait for 100 ns;
    A<="1001";
    B<="1000";
    OP<='0';

    wait for 100 ns;
    A<="1101";
    B<="1110";
    OP<='0';

    wait for 100 ns;
    A<="0001";
    B<="0010";
    OP<='1';

    wait for 100 ns;

```

```

A<="1001";
B<="1000";
OP<='1';

wait for 100 ns;
En<='0';

wait for 100 ns;
En<='1';
A<="1101";
B<="1110";
OP<='1';


wait for 100 ns;
A<="0000";
B<="0111";

wait for 100 ns;
A<="0100";
B<="0011";
wait;


wait;
end process;

end Behavioral;

```

 

- Tri State Buffer – 4 bit

 

-- Module Name: TBuffer_2_1_4Bit - Behavioral

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- 4 bit normal singal controlled tri state buffer
entity TBuffer_2_1_4Bit is
    Port ( B : in STD_LOGIC_VECTOR (3 downto 0);
          C : in STD_LOGIC;
          O : out STD_LOGIC_VECTOR (3 downto 0));
end TBuffer_2_1_4Bit;

architecture Behavioral of TBuffer_2_1_4Bit is

begin

O <= B when C='1' else "ZZZZ";

end Behavioral;
```

- Unit testing and Simulation

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TBuff_4bit_n is
-- Port ( );
end TBuff_4bit_n;


architecture Behavioral of TBuff_4bit_n is
component TBuffer_2_1_4Bit is
    Port ( B : in STD_LOGIC_VECTOR (3 downto 0);
          C : in STD_LOGIC;
          O : out STD_LOGIC_VECTOR (3 downto 0));
end component;
signal B,O : std_logic_vector(3 downto 0);
signal C:std_logic;
begin
UUT:TBuffer_2_1_4Bit port map(B,C,O);
process begin
B<="1111";
C<='1';
```

```


wait for 100 ns;
C<='0';
wait for 100 ns;
C<='1';
wait;

end process;
end Behavioral;

```

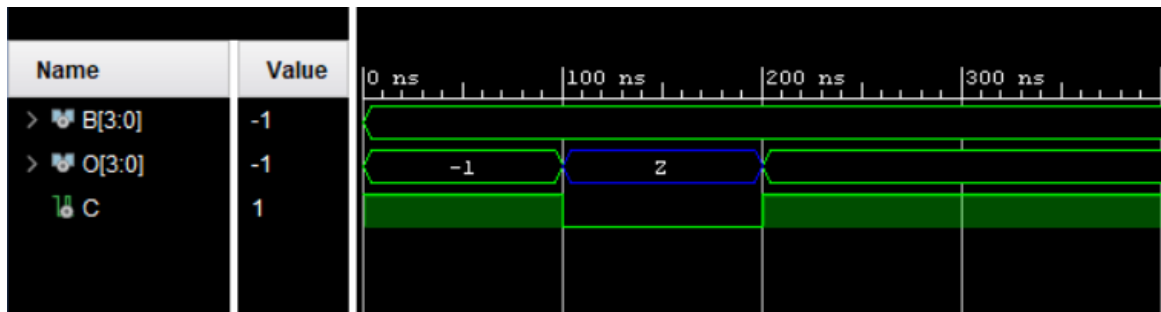

- Tri State Buffer (Inverted) – 4 bit

 

```
-- Module Name: TBuffer_2_1_4Bit_I - Behavioral
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- 4 bit inverted tri state buffer
entity TBuffer_2_1_4Bit_I is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          C : in STD_LOGIC;
          O : out STD_LOGIC_VECTOR (3 downto 0));
end TBuffer_2_1_4Bit_I;

architecture Behavioral of TBuffer_2_1_4Bit_I is
    signal C_invert:std_logic;

begin
    C_invert <= not C;
    O <=A when C_invert='1' else "ZZZZ";

end Behavioral;

```

- Unit testing and Simulation

```


library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Tbuff_4bit_invert is
-- Port ( );
end Tbuff_4bit_invert;
architecture behavioral of Tbuff_4bit_invert is
component TBuffer_2_1_4Bit_I is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          C : in STD_LOGIC;
          O : out STD_LOGIC_VECTOR (3 downto 0));
end component;


signal A,O : std_logic_vector(3 downto 0);
signal C:std_logic;
begin
UUT:TBuffer_2_1_4Bit_I port map(A,C,O);
process begin
A<="1111";
C<='1';
wait for 100 ns;
C<='0';
wait for 100 ns;
C<='1';
wait;

end process;
end Behavioral;

```

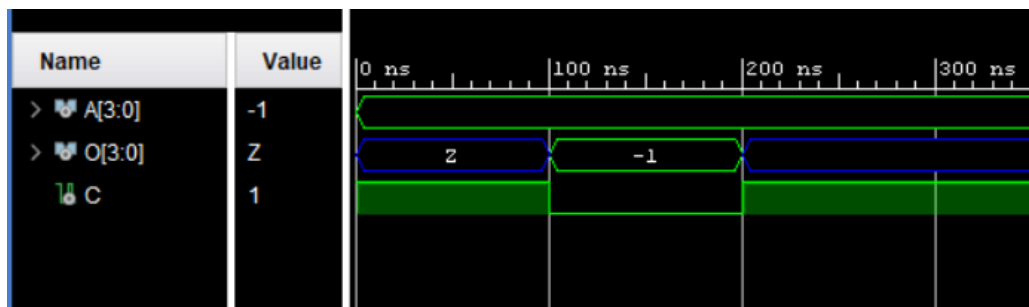

- 2×1 Multiplexer

 

-- Module Name: Mux_2_1 - Behavioral

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- 2 way mux using two inverted and normal signal controlled tri state
buffers
entity Mux_2_1 is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          C : in STD_LOGIC;
          O : out STD_LOGIC_VECTOR (3 downto 0));
end Mux_2_1;

architecture Behavioral of Mux_2_1 is

    component TBuffer_2_1_4Bit_I is
        Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
              C : in STD_LOGIC;
              O : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    component TBuffer_2_1_4Bit is
        Port ( B : in STD_LOGIC_VECTOR (3 downto 0);
              C : in STD_LOGIC;
              O : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    signal A_out,B_out:STD_LOGIC_VECTOR (3 downto 0);

begin

    TBuffer_2_1_4Bit_I_0: TBuffer_2_1_4Bit_I port map(A,C,A_out);
    TBuffer_2_1_4Bit_0: TBuffer_2_1_4Bit PORT MAP(B,C,B_out);
    O <= A_out;

```

```
O <= B_out;


end Behavioral;
```

- Unit testing and Simulation


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Tbuffer_MUX_2_1 is
-- Port ( );
end TB_Tbuffer_MUX_2_1;

architecture Behavioral of TB_Tbuffer_MUX_2_1 is
component Mux_2_1 is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          C : in STD_LOGIC;
          O : out STD_LOGIC_VECTOR (3 downto 0));
end component;
signal A : STD_LOGIC_VECTOR (3 downto 0);
signal B : STD_LOGIC_VECTOR (3 downto 0);
signal C : STD_LOGIC;
signal O : STD_LOGIC_VECTOR (3 downto 0);
begin
UUT:Mux_2_1 port map(A,B,C,O);
process begin
A<="1011";
B<="1111";
C<='1';
wait for 200 ns;
C<='0';
wait for 200 ns;
C<='1';
wait;
end process;
end Behavioral;
```

 

- 8×1 Multiplexer

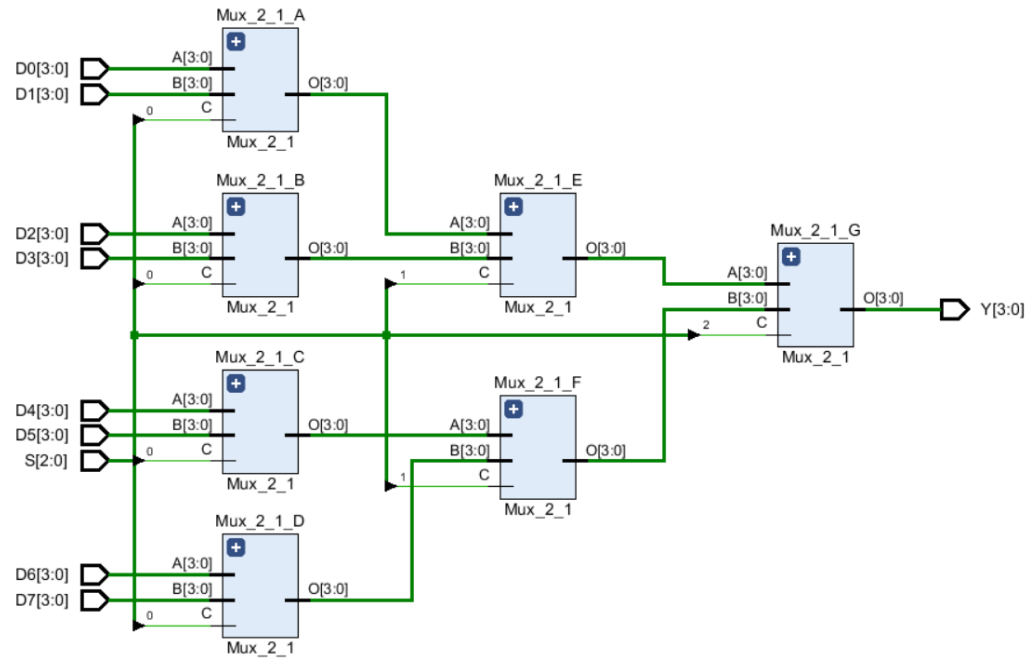

```
-- Module Name: Mux_8_to_1 - Behavioral

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
-- 8 way mux using 2 way mux all in 4 bits
entity Mux_8_to_1 is
    Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
          D0,D1,D2,D3,D4,D5,D6,D7 : in std_logic_vector (3 downto 0);
          Y : out STD_LOGIC_vector(3 downto 0));
end Mux_8_to_1;

architecture Behavioral of Mux_8_to_1 is

    component Mux_2_1 is
        Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
              B : in STD_LOGIC_VECTOR (3 downto 0);
              C : in STD_LOGIC;
              O : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    SIGNAL d12, d23, d45, d67, p, q:STD_LOGIC_VECTOR(3 DOWNTO 0);

begin
    Mux_2_1_A:Mux_2_1
```

```

        port map(D0,D1,S(0),d12);

Mux_2_1_B:Mux_2_1
    port map(D2,D3,S(0),d23);

Mux_2_1_C:Mux_2_1
    port map(D4,D5,S(0),d45);

Mux_2_1_D:Mux_2_1
    port map(D6,D7,S(0),d67);

Mux_2_1_E:Mux_2_1
    port map(d12,d23,S(1),p);

Mux_2_1_F:Mux_2_1
    port map(d45,d67,S(1),q);

Mux_2_1_G:Mux_2_1
    port map(p,q,S(2),Y);

end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_MUX is
-- Port ( );
end TB_MUX;

architecture Behavioral of TB_MUX is

component Mux_8_to_1 is
    Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
          D0,D1,D2,D3,D4,D5,D6,D7 : in std_logic_vector (3 downto 0);

          EN : in STD_LOGIC;
          Y : out STD_LOGIC_vector(3 downto 0));
end component;

signal s:STD_LOGIC_VECTOR (2 downto 0);
signal D0,D1,D2,D3,D4,D5,D6,D7,Y:STD_LOGIC_VECTOR (3 downto 0);
signal EN:STD_LOGIC;

begin

UUT:Mux_8_to_1 port map(s,D0,D1,D2,D3,D4,D5,D6,D7,EN,Y);
process begin
    EN<='1';
    s<="000";
    D0<="0001";
    D1<="0010";
    D2<="0011";
    D3<="0100";
    D4<="0101";

```

```


D5<="0110";
D6<="0111";
D7<="1000";

wait for 100 ns;
s<="001";
wait for 100 ns;
s<="010";
wait for 100 ns;
s<="011";
wait for 100 ns;
s<="100";
wait for 100 ns;
s<="101";
wait for 100 ns;
s<="110";
wait for 100 ns;
s<="111";
wait;


end process;

end Behavioral;

```

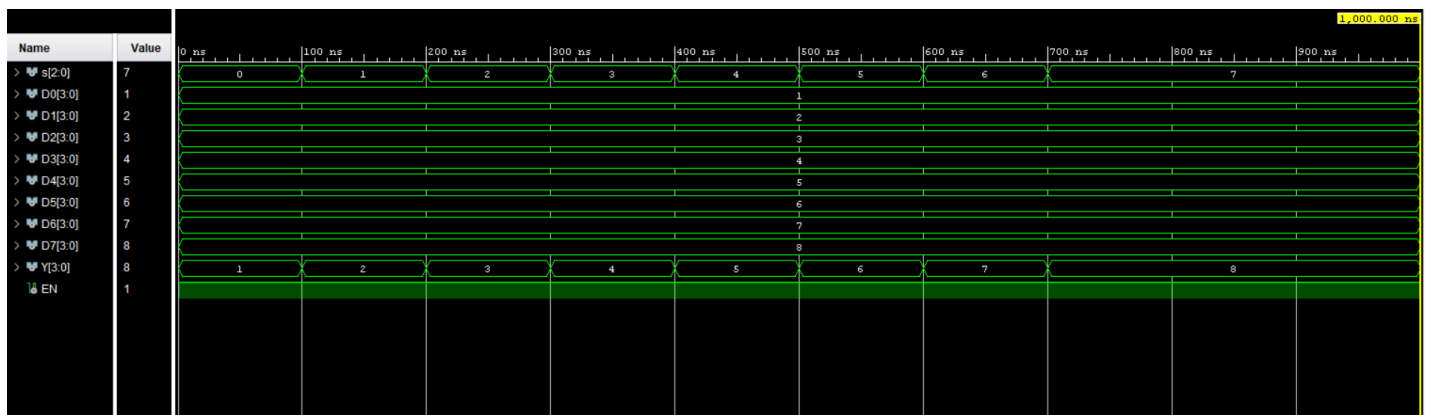

- Mux Selector

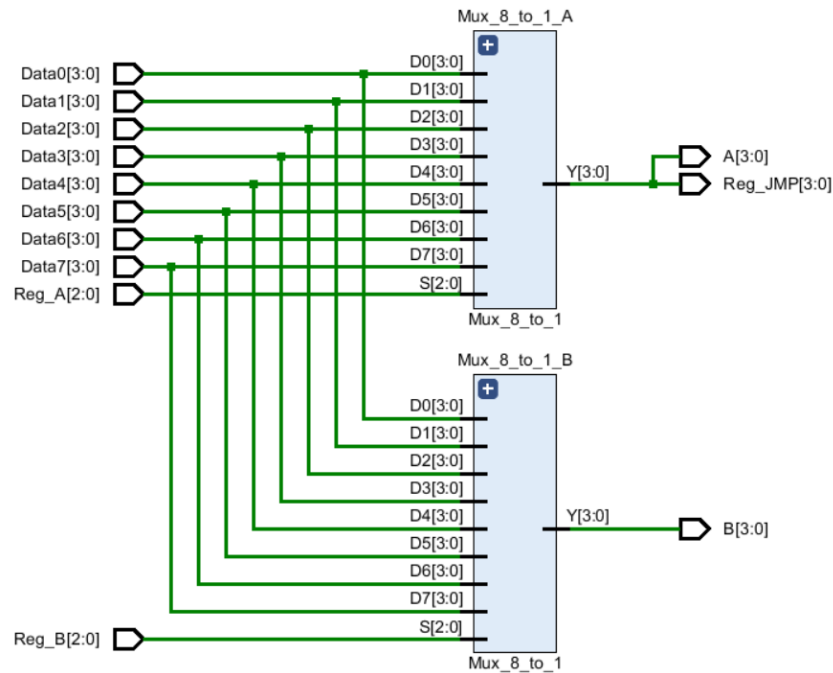

```
-- Module Name: Mux_Selector - Behavioral
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- Use Register select signal for A and B Register and get value
```

```
entity Data_Bus is
```

```
    Port ( Data0 : in STD_LOGIC_VECTOR (3 downto 0);
          Data1 : in STD_LOGIC_VECTOR (3 downto 0);
          Data2 : in STD_LOGIC_VECTOR (3 downto 0);
          Data3 : in STD_LOGIC_VECTOR (3 downto 0);
          Data4 : in STD_LOGIC_VECTOR (3 downto 0);
          Data5 : in STD_LOGIC_VECTOR (3 downto 0);
          Data6 : in STD_LOGIC_VECTOR (3 downto 0);
          Data7 : in STD_LOGIC_VECTOR (3 downto 0);
          Reg_A : in STD_LOGIC_VECTOR (2 downto 0);
          Reg_B : in STD_LOGIC_VECTOR (2 downto 0);
          Reg_JMP : out STD_LOGIC_vector (3 downto 0);
          A : out STD_LOGIC_VECTOR (3 downto 0);
          B : out STD_LOGIC_VECTOR (3 downto 0));
```

```
end Data_Bus;
```

```
architecture Behavioral of Data_Bus is
```

```
    component Mux_8_to_1 is
```

```
        Port ( S : in STD_LOGIC_VECTOR (2 downto 0);
              D0,D1,D2,D3,D4,D5,D6,D7 : in std_logic_vector (3 downto 0);
              Y : out STD_LOGIC_vector(3 downto 0));
```

```
    end component;
```

```
    signal register_A:std_logic_vector (3 downto 0);
```

```
begin
```

```

    Mux_8_to_1_A:Mux_8_to_1 port
map (Reg_A,Data0,Data1,Data2,Data3,Data4,Data5,Data6,Data7,register_A);
    Mux_8_to_1_B:Mux_8_to_1 port
map (Reg_B,Data0,Data1,Data2,Data3,Data4,Data5,Data6,Data7,B);
    A <= register_A;
    Reg_JMP <= register_A;

end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_MUXselector is
-- Port ( );
end TB_MUXselector;

architecture Behavioral of TB_MUXselector is

component Data_Bus is
    Port ( Data0 : in STD_LOGIC_VECTOR (3 downto 0);
          Data1 : in STD_LOGIC_VECTOR (3 downto 0);
          Data2 : in STD_LOGIC_VECTOR (3 downto 0);
          Data3 : in STD_LOGIC_VECTOR (3 downto 0);
          Data4 : in STD_LOGIC_VECTOR (3 downto 0);
          Data5 : in STD_LOGIC_VECTOR (3 downto 0);
          Data6 : in STD_LOGIC_VECTOR (3 downto 0);
          Data7 : in STD_LOGIC_VECTOR (3 downto 0);
          Reg_A : in STD_LOGIC_VECTOR (2 downto 0);
          Reg_B : in STD_LOGIC_VECTOR (2 downto 0);
          Reg_JMP : out STD_LOGIC_vector (3 downto 0);
          A : out STD_LOGIC_VECTOR (3 downto 0);
          B : out STD_LOGIC_VECTOR (3 downto 0));
end component;

signal Data0 : STD_LOGIC_VECTOR (3 downto 0);
signal Data1 : STD_LOGIC_VECTOR (3 downto 0);
signal Data2 : STD_LOGIC_VECTOR (3 downto 0);
signal Data3 : STD_LOGIC_VECTOR (3 downto 0);
signal Data4 : STD_LOGIC_VECTOR (3 downto 0);
signal Data5 : STD_LOGIC_VECTOR (3 downto 0);
signal Data6 : STD_LOGIC_VECTOR (3 downto 0);
signal Data7 : STD_LOGIC_VECTOR (3 downto 0);
signal Reg_A : STD_LOGIC_VECTOR (2 downto 0);
signal Reg_B : STD_LOGIC_VECTOR (2 downto 0);
signal Reg_JMP : STD_LOGIC_vector (3 downto 0);
signal A : STD_LOGIC_VECTOR (3 downto 0);
signal B : STD_LOGIC_VECTOR (3 downto 0);

begin
    UUT:Data_Bus port
map (Data0,Data1,Data2,Data3,Data4,Data5,Data6,Data7,Reg_A,Reg_B,Reg_JMP,A,B);

process begin


```

```


Data0<="0001";
Data1<="0010";
Data2<="0011";
Data3<="0100";
Data4<="0101";
Data5<="0110";
Data6<="0111";
Data7<="1000";
Reg_A<="000";
wait for 100 ns;
Reg_B<="001";
wait for 100 ns;
Reg_A<="010";
Reg_B<="011";
wait for 100 ns;
Reg_A<="101";
Reg_B<="111";
wait for 100 ns;
Reg_A<="101";
Reg_B<="111";
end process;

end Behavioral;

```

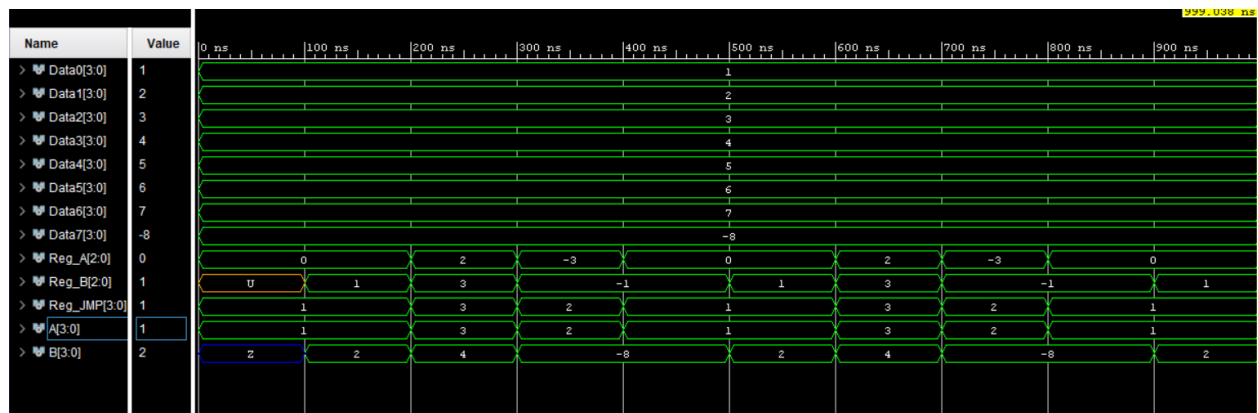

- Register

 

-- Module Name: Reg - Behavioral

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Reg is
    Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
          En : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (3 downto 0));
end Reg;

architecture Behavioral of Reg is
begin
    -- Process triggered by the clock signal
    process (Clk)
    begin
        if (rising_edge(Clk)) then -- Check for rising edge of the clock
            if En = '1' then -- Check if enable signal is active
                Q <= D; -- Transfer input D to output Q
            end if;
        end if;
    end process;
end Behavioral;
```

- Unit testing and Simulation

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_REG is
    -- Port ( );
end TB_REG;

architecture Behavioral of TB_REG is
    COMPONENT Reg is
        Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
              En : in STD_LOGIC;
              Clk : in STD_LOGIC;
```


```

        Q : out STD_LOGIC_VECTOR (3 downto 0));
end COMPONENT;
COMPONENT Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
           Clk_out : out STD_LOGIC);
end COMPONENT;


SIGNAL D : STD_LOGIC_VECTOR (3 downto 0);
SIGNAL En : STD_LOGIC;
SIGNAL Clk_in, Clk_out: STD_LOGIC;
SIGNAL Q : STD_LOGIC_VECTOR (3 downto 0);
begin
    UUT:Reg PORT MAP(D,En,Clk_out,Q);
    UUT1:Slow_Clk PORT MAP(Clk_in,Clk_out);
    PROCESS BEGIN
        Clk_in<='1';
        wait for 3 ns;
        Clk_in<='0';
        wait for 3 ns;
        end process;
    process begin
        D<="1001";
        En<='1';
        wait for 100 ns;
        En<='0';
        wait for 100 ns;
        D<="1111";
        En<='1';
        wait for 100 ns;
        En<='0';
        END PROCESS;

    end Behavioral;

```

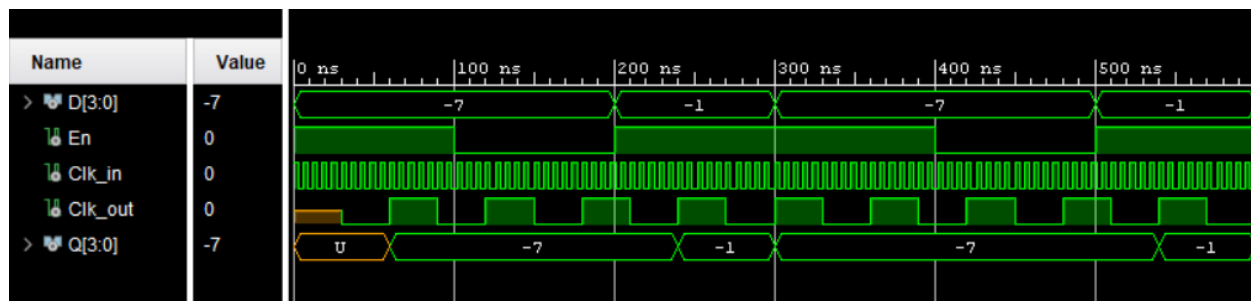

- 2 to 4 Decoder

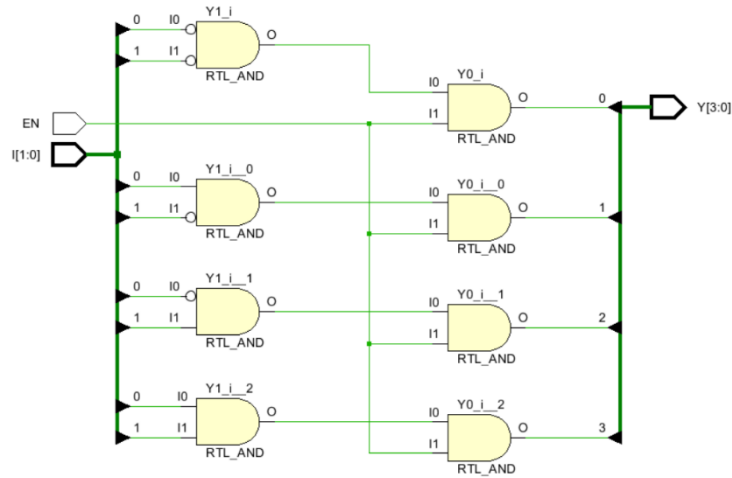

-- Module Name: Decoder_2_to_4 - Behavioral

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_2_to_4 is
    Port (
        I : in STD_LOGIC_VECTOR(1 downto 0); -- Input signal
        EN : in STD_LOGIC; -- Enable signal
        Y : out STD_LOGIC_VECTOR(3 downto 0) -- Output signals
    );
end Decoder_2_to_4;

architecture Behavioral of Decoder_2_to_4 is
    -- Decode input I based on EN signal to produce a 4-bit output
    Y(0) <= (NOT I(0)) AND (NOT I(1)) AND EN; -- Active when I = "00" and EN
is high
    Y(1) <= I(0) AND (NOT I(1)) AND EN; -- Active when I = "01" and EN
is high
    Y(2) <= (NOT I(0)) AND I(1) AND EN; -- Active when I = "10" and EN
is high
    Y(3) <= I(0) AND I(1) AND EN; -- Active when I = "11" and EN
is high
end Behavioral;

```

- Unit testing and Simulation

```


library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Dec2to4 is
-- Port ( );
end TB_Dec2to4;


architecture Behavioral of TB_Dec2to4 is
component Decoder_2_to_4 is
    Port (
        I : in STD_LOGIC_VECTOR(1 downto 0); -- Input signal
        EN : in STD_LOGIC; -- Enable signal
        Y : out STD_LOGIC_VECTOR(3 downto 0) -- Output signals
    );
end component;
signal I : STD_LOGIC_VECTOR(1 downto 0);
signal EN : STD_LOGIC;
signal Y : STD_LOGIC_VECTOR(3 downto 0);
begin
UUT:Decoder_2_to_4 port map(I,EN,Y);
process begin
I<="00";
EN<='0';
WAIT FOR 100 NS;
EN<='1';
WAIT FOR 100 NS;
I<="01";
WAIT FOR 100 NS;
I<="10";
WAIT FOR 100 NS;
I<="11";
WAIT FOR 100 NS;
I<="00";
EN<='0';
wait;
end process;

end Behavioral;

```

 

- 3 to 8 Decoder

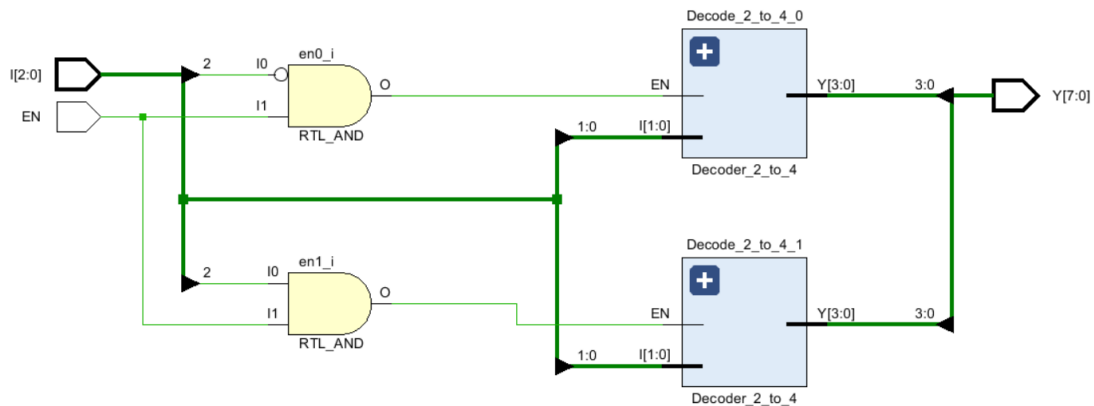

-- Module Name: Decoder_3_to_8 - Behavioral

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_3_to_8 is

Port (

I : in STD_LOGIC_VECTOR (2 downto 0); -- 3-bit input

EN : in STD_LOGIC; -- Enable input

Y : out STD_LOGIC_VECTOR (7 downto 0) -- 8-bit output

);

end Decoder_3_to_8;

architecture Behavioral of Decoder_3_to_8 is

COMPONENT Decoder_2_to_4

PORT(I:IN STD_LOGIC_VECTOR;

EN:IN STD_LOGIC;

Y:OUT STD_LOGIC_VECTOR);

END COMPONENT;

signal I0, I1 : STD_LOGIC_VECTOR(1 downto 0); -- Signals for the inputs of the nested decoders

signal Y0, Y1 : STD_LOGIC_VECTOR(3 downto 0); -- Signals for the outputs of the nested decoders

signal en0, en1, I2 : STD_LOGIC; -- Enable signals for the nested decoders and intermediate bit signal

begin

Decode_2_to_4_0 :Decoder_2_to_4

port map(

I => I0,

EN => en0,

Y => Y0

);

Decode_2_to_4_1 : Decoder_2_to_4

port map(


```

        I => I1,
        EN => en1,
        Y => Y1
    );

    -- Assignments for enable signals and connecting inputs to outputs
    en0 <= NOT(I(2)) AND EN;
    en1 <= I(2) AND EN;
    I0 <= I(1 downto 0);
    I1 <= I(1 downto 0);
    I2 <= I(2);
    Y(3 downto 0) <= Y0;
    Y(7 downto 4) <= Y1;

end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_DEC3TO8 is
    -- Port ( );
end TB_DEC3TO8;

architecture Behavioral of TB_DEC3TO8 is
    COMPONENT Decoder_3_to_8 is
        Port (
            I : in STD_LOGIC_VECTOR (2 downto 0); -- 3-bit input
            EN : in STD_LOGIC; -- Enable input
            Y : out STD_LOGIC_VECTOR (7 downto 0) -- 8-bit output
        );
    end COMPONENT;

    SIGNAL I : STD_LOGIC_VECTOR (2 downto 0);
    SIGNAL EN : STD_LOGIC;
    SIGNAL Y : STD_LOGIC_VECTOR (7 downto 0);
begin
    UUT:Decoder_3_to_8 PORT MAP(I,EN,Y);
    PROCESS BEGIN
        I<="000";
        EN<='0';
        WAIT FOR 100 NS;
        EN<='1';
        WAIT FOR 100 NS;
        I<="001";
        WAIT FOR 100 NS;
        I<="010";
        WAIT FOR 100 NS;
        I<="011";
        WAIT FOR 100 NS;
        I<="100";
        WAIT FOR 100 NS;
        I<="101";
        WAIT FOR 100 NS;
        I<="110";
    end PROCESS;
end TB_DEC3TO8;


```

```


WAIT FOR 100 NS;
I<="111";
END PROCESS;

end Behavioral;

```

 

- Register Bank

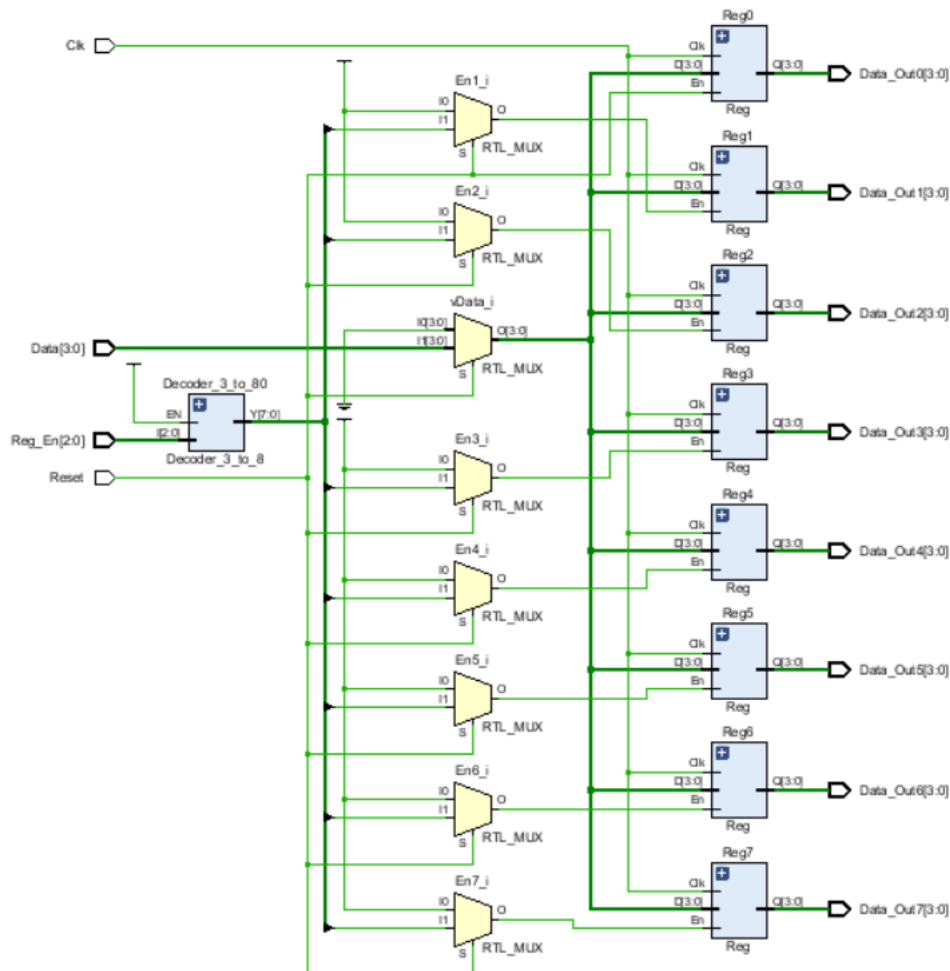

```

-- Module Name: Reg_Bank - Behavioral

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

entity Reg_Bank is
    Port ( Clk : in STD_LOGIC;
          Reset : in STD_LOGIC;
          Reg_En : in STD_LOGIC_VECTOR (2 downto 0);
          Data : in STD_LOGIC_VECTOR (3 downto 0);
          Data_Out0 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out1 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out2 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out3 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out4 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out5 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out6 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out7 : out STD_LOGIC_VECTOR (3 downto 0));

end Reg_Bank;

architecture Behavioral of Reg_Bank is
    component Reg is
        Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
              En : in STD_LOGIC;
              Clk : in STD_LOGIC;
              Q : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    component Decoder_3_to_8 is
        Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
              EN : in STD_LOGIC;
              Y : out STD_LOGIC_VECTOR (7 downto 0));
    end component;

    signal Dec_out : STD_LOGIC_VECTOR (7 downto 0);
    signal En0,En1,En2,En3,En4,En5,En6,En7 : std_logic;
    signal vData,vData_Out7 : std_logic_vector (3 downto 0);

begin
    -- Assign 0000 in all register when reset button pushed
    vData<= "0000" when (Reset='1') else Data;
    En0<= '1' when (Reset='1') else '0';
    En1<= '1' when (Reset='1') else Dec_out(1);
    En2<= '1' when (Reset='1') else Dec_out(2);
    En3<= '1' when (Reset='1') else Dec_out(3);
    En4<= '1' when (Reset='1') else Dec_out(4);
    En5<= '1' when (Reset='1') else Dec_out(5);
    En6<= '1' when (Reset='1') else Dec_out(6);
    En7<= '1' when (Reset='1') else Dec_out(7);
    Decoder_3_to_80:Decoder_3_to_8 port map(Reg_En,'1',Dec_out);
    Reg0:Reg port map(vData,En0,Clk,Data_Out0);
    Reg1:Reg port map(vData,En1,Clk,Data_Out1);
    Reg2:Reg port map(vData,En2,Clk,Data_Out2);

```

```

Reg3:Reg port map(vData,En3,Clk,Data_Out3);
Reg4:Reg port map(vData,En4,Clk,Data_Out4);
Reg5:Reg port map(vData,En5,Clk,Data_Out5);
Reg6:Reg port map(vData,En6,Clk,Data_Out6);
Reg7:Reg port map(vData,En7,Clk,vData_Out7);
-- output R7 register for used in led sevens segment display
Data_Out7<=vData_Out7;

end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Reg_Bank is
-- Port ( );
end TB_Reg_Bank;

architecture Behavioral of TB_Reg_Bank is
component Reg_Bank is
    Port ( Clk : in STD_LOGIC;
          Reset : in STD_LOGIC;
          Reg_En : in STD_LOGIC_VECTOR (2 downto 0);
          Data : in STD_LOGIC_VECTOR (3 downto 0);
          Data_Out0 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out1 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out2 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out3 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out4 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out5 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out6 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out7 : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC);
end component;

signal regen: std_logic_vector (2 downto 0);
signal data , out0,out1,out2,out3,out4,out5,out6,out7 : std_logic_vector(3
downto 0);
signal clk_in,clk_out,Reset : std_logic;
begin
    UUT_sc:Slow_Clk port map(clk_in,clk_out);
    UUT_rb:Reg_Bank port
map(clk_out,Reset,regen,data,out0,out1,out2,out3,out4,out5,out6,out7);

process begin
    clk_in<='1';
    wait for 3 ns;
    clk_in<='0';
    wait for 3 ns;
end process;


```

```


process begin
Reset<='1';
wait for 100 ns;
Reset<='0';
wait for 100 ns;
Data<="1010";
regen<="000";
wait for 100 ns;
regen<="001";
wait for 100 ns;
regen<="010";
wait for 100 ns;
regen<="011";
wait for 100 ns;
regen<="100";
wait for 100 ns;
regen<="101";
wait for 100 ns;
regen<="110";
wait for 100 ns;
regen<="111";
wait;

end process;
end Behavioral;

```

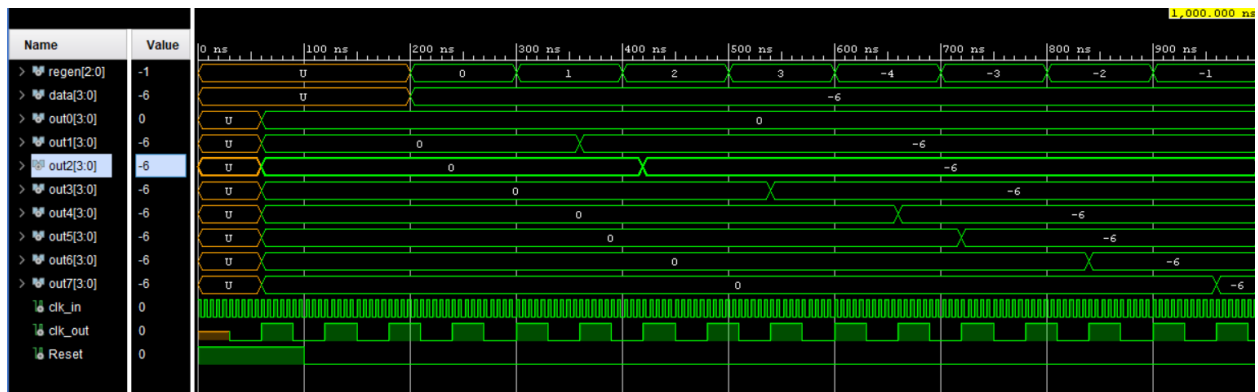

- Load Selector MUX

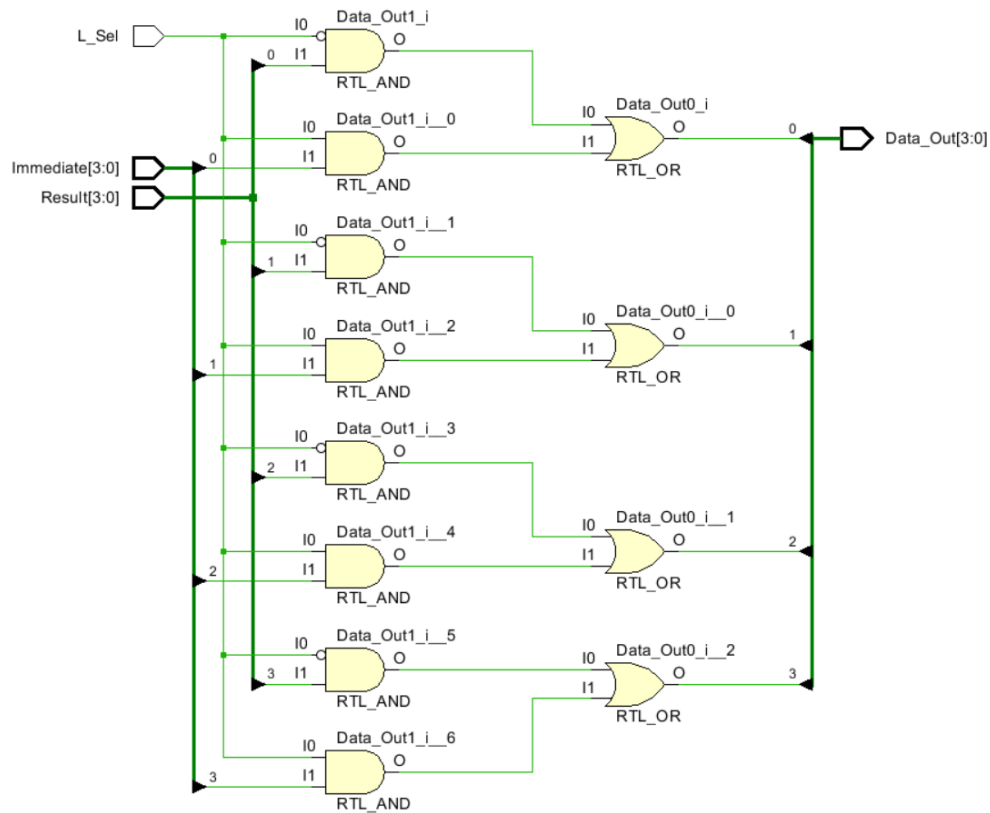

-- Module Name: MUX_2_way_4 - Behavioral

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- 2 way 4 bit mux as load selector

entity MUX_2_way_4 is

Port (

data Immediate : in STD_LOGIC_VECTOR (3 downto 0); -- Immediate input

Result : in STD_LOGIC_VECTOR (3 downto 0); -- Result input data

L_Sel : in STD_LOGIC; -- Selector input

Data_Out : out STD_LOGIC_VECTOR (3 downto 0) -- Output data

);

end MUX_2_way_4;

architecture Behavioral of MUX_2_way_4 is

-- Logic to determine output based on selector L_Sel

begin

Data_Out(0) <= (not L_Sel and Result(0)) or (L_Sel and Immediate(0));

Data_Out(1) <= (not L_Sel and Result(1)) or (L_Sel and Immediate(1));

Data_Out(2) <= (not L_Sel and Result(2)) or (L_Sel and Immediate(2));

Data_Out(3) <= (not L_Sel and Result(3)) or (L_Sel and Immediate(3));

end Behavioral;

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_MUX_4_T_Buf is
-- Port ( );
end TB_MUX_4_T_Buf;

architecture Behavioral of TB_MUX_4_T_Buf is


component MUX_2_way_4 is
    Port ( Immediate : in STD_LOGIC_VECTOR (3 downto 0);
          Result      : in STD_LOGIC_VECTOR (3 downto 0);
          L_Sel       : in STD_LOGIC;
          Data_Out     : out STD_LOGIC_VECTOR (3 downto 0));
end component;

signal A,B : STD_LOGIC_VECTOR (3 downto 0);
signal C : STD_LOGIC;
signal O : STD_LOGIC_VECTOR (3 downto 0); -- Initialize 0

begin
UUT: MUX_2_way_4 port map(Immediate=>A,Result => B, L_Sel => C, Data_Out =>
O);

process
begin
    A<="1010";
    B<="1110";
    C<='1';
    wait for 500 ns;
    C<='0';
    wait;
end process;
end Behavioral;

```

 

- Instruction Decoder



-- Module Name: Instruction_Dec - Behavioral

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

entity Instruction_Dec is
    Port ( Ins : in STD_LOGIC_VECTOR (13 downto 0);
          Reg_JMP : in STD_LOGIC_VECTOR (3 downto 0);
          L_Sel : out STD_LOGIC;
          Immediate : out STD_LOGIC_VECTOR (3 downto 0);
          Reg_Sel_A : out STD_LOGIC_VECTOR (2 downto 0);
          Reg_Sel_B : out STD_LOGIC_VECTOR (2 downto 0);
          A_S_Sel : out STD_LOGIC;
          Reg_En : out STD_LOGIC_VECTOR (2 downto 0);
          JMP_F : out STD_LOGIC;
          JMP_Add : out STD_LOGIC_VECTOR (2 downto 0);
          A_S_En:out std_logic);
end Instruction_Dec;

architecture Behavioral of Instruction_Dec is

    signal insts:std_logic_vector(3 downto 0);
    signal regA,regB:std_logic_vector(2 downto 0);

    --signal value:std_logic_vector(3 downto 0);

```



```

signal
vJMP_F,v1L_Sel,v2L_Sel,default_L_Sel,v1A_S_Sel,v2A_S_Sel,v3A_S_Sel:std_logic;
signal vReg_En,default_vector,vReg_Sel_B,vReg_Sel_A:std_logic_vector(2 downto
0);

begin
    -- Decode the instruction
    Immediate <= Ins(3 downto 0); -- This is always directly decoded from Ins
    insts <= Ins(13 downto 10); --OP_code extraction
    regA <= Ins(9 downto 7);      -- Register A signal extraction
    regB <= Ins(6 downto 4);      -- Register B signal extraction
    Reg_En<=regA;                -- Register enable output extraction

    -- Load selector between immediate and Adder/Subtractor output
    -- Load selector '0' output selection
    v1L_Sel<=not(insts(3) or insts(2) or insts(1)) or ( not(insts(3) or
insts(1) or insts(0)) and insts(2) );
    -- Undefine Load selector output when not '0' using undefined signal
    v2L_Sel<=not v1L_Sel when (v1L_Sel='1') else default_L_Sel;
    -- Assign '1' to load selector for suitable operations. So It will only
    output '1' and '0' for preferred instructions and undefined at other
    instructions
    L_Sel <= insts(1) and not (insts(3) or insts(2) or insts(0))
when(insts(1)='1' and insts(3)='0' and insts(2)='0' and insts(0)='0') else
v2L_Sel;

    -- JMP_Flag output
    JMP_F <= ( NOT(insts(3)) AND not insts(2) AND insts(1) AND (insts(0)) AND
( NOT ( Reg_JMP(3) or Reg_JMP(2) or Reg_JMP(1) or Reg_JMP(0) )) OR (not
insts(3) AND insts(2) AND insts(1) AND NOT(insts(0))));

    -- JMP_Address get by last 3 bits
    JMP_Add<=Ins(2 downto 0);

    -- RegSel_A output to give to Register select from register bank to give
    input to Adder/Subtractor
    vReg_Sel_A<="000" when ((not(insts(3) or insts(2) or insts(1)) and
insts(0))='1') else default_vector;
    Reg_Sel_A <= regA when (NOT insts(3) AND (( not insts(1) and not
insts(0)) or (not insts(2)and insts(1) and insts(0) ) )='1' else vReg_Sel_A;

    -- Reg_Selector for B
    -- Get regA or undefined to a signal. For RegA for RegA selecting moments
    and others as undefined
    vReg_Sel_B<=regA when (NOT(insts(3)) AND NOT(insts(2)) AND NOT insts(1)
AND (insts(0)))='1' else default_vector;
    -- Get regB or regA or undefined as suitable
    Reg_Sel_B <=regB when (NOT(insts(3)) AND NOT(insts(1)) AND NOT(insts(0))
AND (insts(2) or not insts(2)))='1' else vReg_Sel_B;

    --Adder Subtractor Selector
    v1A_S_Sel<= not (insts(3) or insts(2) or insts(1) or insts(0));
    v2A_S_Sel<= not v1A_S_Sel when (v1A_S_Sel='1') else default_L_Sel;
    v3A_S_Sel <= (NOT(insts(3)) AND NOT(insts(1)) and (insts(2) xor
insts(0)));
    A_S_Sel<= v3A_S_Sel when (v3A_S_Sel='1') else v2A_S_Sel;
    A_S_En<=NOT(insts(3) or insts(1) or insts(0));

```

```
end Behavioral;
```

- Unit testing and Simulation

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Ins is
-- Port ( );
end TB_Ins;
architecture Behavioral of TB_Ins is
component Instruction_Dec is
    Port ( Ins : in STD_LOGIC_VECTOR (13 downto 0);
          Reg_JMP : in STD_LOGIC_VECTOR (3 downto 0);
          L_Sel : out STD_LOGIC;
          Immediate : out STD_LOGIC_VECTOR (3 downto 0);
          Reg_Sel_A : out STD_LOGIC_VECTOR (2 downto 0);
          Reg_Sel_B : out STD_LOGIC_VECTOR (2 downto 0);
          A_S_Sel : out STD_LOGIC;
          Reg_En : out STD_LOGIC_VECTOR (2 downto 0);
          JMP_F : out STD_LOGIC;
          JMP_Add : out STD_LOGIC_VECTOR (2 downto 0));
end component;

signal Ins:STD_LOGIC_VECTOR (13 downto 0);
signal Reg_En,Reg_Sel_A,Reg_Sel_B,JMP_Add:STD_LOGIC_VECTOR (2 downto 0);
signal Immediate,Reg_JMP:STD_LOGIC_VECTOR (3 downto 0);
signal JMP_F,L_Sel,A_S_Sel:STD_LOGIC;


begin
    UUT:Instruction_Dec port
    map(Ins=>Ins,A_S_Sel=>A_S_Sel,L_Sel=>L_Sel,Reg_JMP=>Reg_JMP,Reg_En=>Reg_En,Immediate=>Immediate,Reg_Sel_A=>Reg_Sel_A,Reg_Sel_B=>Reg_Sel_B,JMP_F=>JMP_F,JMP_Add=>JMP_Add);

    process begin
        Ins<="00101010000110";
        wait for 100 ns;
        Ins<="00101111010001";
        wait for 100 ns;
        Ins<="00101100000100";
        wait for 100 ns;
        Ins<="00001111100000";
        wait for 100 ns;
        Reg_JMP<="0000";
        Ins<="00111110000001";
        wait for 100 ns;
        Ins<="00100000000001";
        wait for 100 ns;
        Ins<="00001110000000";
        wait for 100 ns;
        Ins<="01001111000000";
        wait for 100 ns;
        Ins<="01010000000000";
        wait for 100 ns;
        Ins<="01100000000100";
```


```

        wait for 100 ns;
    end process;
end Behavioral;

```

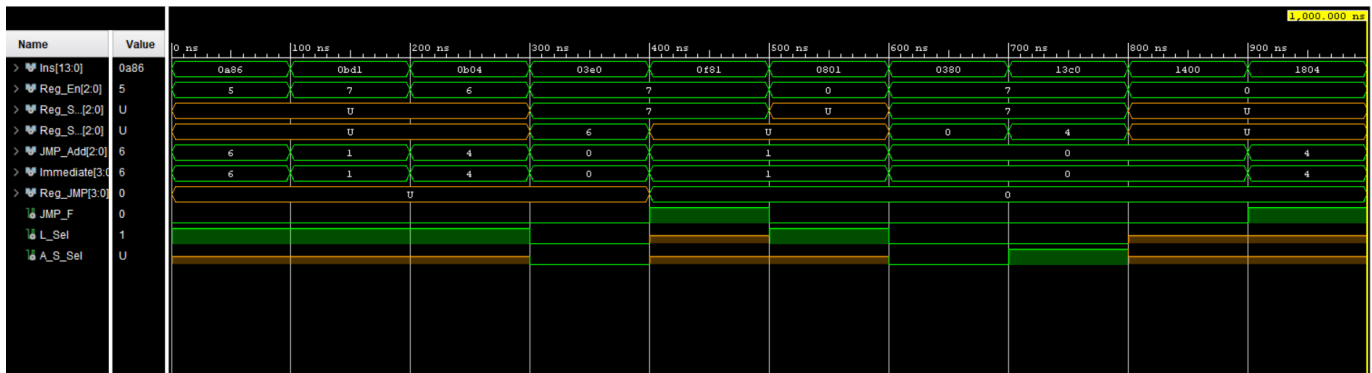

- Program ROM

 

```
-- Module Name: Program_Rom - Behavioral
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

```

```

entity Program_Rom is
    Port ( M_Sel : in STD_LOGIC_VECTOR (2 downto 0);
          Ins : out STD_LOGIC_VECTOR (13 downto 0));
end Program_Rom;

```

```
architecture Behavioral of Program_Rom is
```

```
--          Instructions          --
```

```

-- NAME OP_CODE REG_A REG_B VALUE Description
-- movi   0010   111   000  1010  Move value to Register A
-- add    0000   111   101  0000  Final result will be saved in Register A
-- neg    0001   111   000  0000  Negative in two's complement is stored in
Register A
-- JZR    0011   111   000  0101  If Register A's value is Zero then jump to
instruction given by last 3 bit
-- sub    0100   111   101  0000  Subtract Register B's value from Register A
and stored in Register A
-- NOP    0101   000   000  0000  Pass clock cycle and do nothing

```

```
-- JMP      0110  000   000  0111   Jump to the instruction given by last 3
bits
```

```
type rom_type is array (0 to 7) of std_logic_vector(13 downto 0);
signal Instruction_ROM : rom_type := (
  "00100000000111", -- 000
  "00101110000101", -- 001
  "00001110000000", -- 010
  "00100000001001", -- 011
  "00101110001011", -- 100
  "00001110000000", -- 101
  "01010000000110", -- 110
  "00100110001001"); -- 111
begin

Ins<=Instruction_ROM(to_integer(unsigned(M_Sel)));
end Behavioral;
```

- Unit testing and Simulation

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_programrom is
-- Port ( );
end TB_programrom;

architecture Behavioral of TB_programrom is
component Program_Rom is
  Port ( M_Sel : in STD_LOGIC_VECTOR (2 downto 0);
        Ins : out STD_LOGIC_VECTOR (13 downto 0));
end component;
signal M_Sel:std_logic_vector(2 downto 0);
signal Ins:std_logic_vector(13 downto 0);
begin
UUT:Program_Rom port map(M_Sel,Ins);
process begin
M_Sel<="000";
wait for 100 ns;
M_Sel<="001";
wait for 100 ns;
M_Sel<="010";
wait for 100 ns;
M_Sel<="011";
wait for 100 ns;
M_Sel<="100";
wait for 100 ns;
M_Sel<="101";
wait for 100 ns;
M_Sel<="110";
wait for 100 ns;
M_Sel<="111";
wait for 100 ns;
M_Sel<="001";
wait for 100 ns;
```


```

end process;
end Behavioral;

```

Name	Value	0 ns	100 ns	200 ns	300 ns	400 ns	500 ns	600 ns	700 ns	800 ns
> M_Sel[2:0]	001	000	001	010	011	100	101	110	111	001
> Ins[13:0]	0010001	001000000000	001000100000	001011100000	000011100000	000011100100	000111100000	001101000000	001001110010	001000100000

- Tri State Buffer – 3bit

 

```
-- Module Name: TBuffer_3_Bit - Behavioral
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TBuffer_3_Bit is
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
          C : in STD_LOGIC;
          O : out STD_LOGIC_VECTOR (2 downto 0));
end TBuffer_3_Bit;

architecture Behavioral of TBuffer_3_Bit is

begin
    O<=A when (C='1') else "ZZZ";

end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Tri_normal is
-- Port ( );
end TB_Tri_normal;

```

```

architecture Behavioral of TB_Tri_normal is
component TBuffer_3_Bit is
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
          C : in STD_LOGIC;
          O : out STD_LOGIC_VECTOR (2 downto 0));
end component;


signal A,O:STD_LOGIC_VECTOR (2 downto 0);
signal C:std_logic;

begin
UUT:TBuffer_3_Bit port map(A,C,O);


process begin
    A<="111";
    C<='1';
    wait for 100 ns;
    A<="101";
    C<='0';
    wait;
end process;

end Behavioral;

```

 

- Tri State Buffer (Inverted) – 3bit

 

-- Module Name: TBuffer_3_Bit_I - Behavioral

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TBuffer_3_Bit_I is
    Port ( B : in STD_LOGIC_VECTOR (2 downto 0);

```

```

        C : in STD_LOGIC;
        O : out STD_LOGIC_VECTOR (2 downto 0));
end TBuffer_3_Bit_I;

architecture Behavioral of TBuffer_3_Bit_I is

    signal c_invert:std_logic;
begin
    c_invert <= not C;
    O <=B when (c_invert='1') else "ZZZ";
end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_Tri_Invert is
-- Port ( );
end TB_Tri_Invert;

architecture Behavioral of TB_Tri_Invert is

    component TBuffer_3_Bit_I is
        Port ( B : in STD_LOGIC_VECTOR (2 downto 0);
              C : in STD_LOGIC;
              O : out STD_LOGIC_VECTOR (2 downto 0));
    end component;

    signal A,O:STD_LOGIC_VECTOR (2 downto 0);
    signal C:std_logic;


begin
    UUT:TBuffer_3_Bit_I port map(A,C,O);

    process begin
        A<="111";
        C<='1';
        wait for 200 ns;
        A<="101";
        C<='0';
        wait for 200 ns;


    end process;

end Behavioral;

```

 

- 2×1 Multiplexer – 3 bit

 

```
-- Module Name: TBUFFER_2_way_3 - Behavioral
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
-- 2 way mux using 2 tri state buffers
```

```
entity TBUFFER_2_way_3 is
```

```
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          B : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          C : in STD_LOGIC;
```

```
          O : out STD_LOGIC_VECTOR (2 downto 0));
```

```
end TBUFFER_2_way_3;
```

```
architecture Behavioral of TBUFFER_2_way_3 is
```

```
-- Non inverted control tristate buffer to output the same input under '1' signal
```

```
component TBUFFER_3_Bit is
```

```
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          C : in STD_LOGIC;
```

```
          O : out STD_LOGIC_VECTOR (2 downto 0));
```

```
end component;
```

```
-- Inverted control tristate buffer to output the same input under '0' signal
```

```
component TBUFFER_3_Bit_I is
```

```
    Port ( B : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          C : in STD_LOGIC;
```

```
          O : out STD_LOGIC_VECTOR (2 downto 0));
```

```
end component;
```

```
signal A_out,B_out:STD_LOGIC_VECTOR (2 downto 0);
```

```
begin
```

```
TBUFFER_3_Bit_1:TBUFFER_3_Bit port map(B,C,B_out);
```

```
TBUFFER_3_Bit_I_1:TBUFFER_3_Bit_I PORT MAP(A,C,A_out);
```

```
O<= A_out;
```

```
O<= B_out;
```

```
end Behavioral;
```


- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_tristate is
-- Port ( );
end TB_tristate;


architecture Behavioral of TB_tristate is
component TBuffer_2_way_3 is
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
          B : in STD_LOGIC_VECTOR (2 downto 0);
          C : in STD_LOGIC;
          O : out STD_LOGIC_VECTOR (2 downto 0));
end component;

signal A,B : STD_LOGIC_VECTOR (2 downto 0);
signal C : STD_LOGIC;
signal O : STD_LOGIC_VECTOR (2 downto 0); -- Initialize O


begin
UUT: TBuffer_2_way_3 port map(A=>A,B => B, C => C, O => O);

process
begin
A<="101";
B<="111";
C<='1';
wait for 500 ns;
C<='0';
wait;
end process;
end Behavioral;

```

 

- Ripple Carry Adder – 3 bit

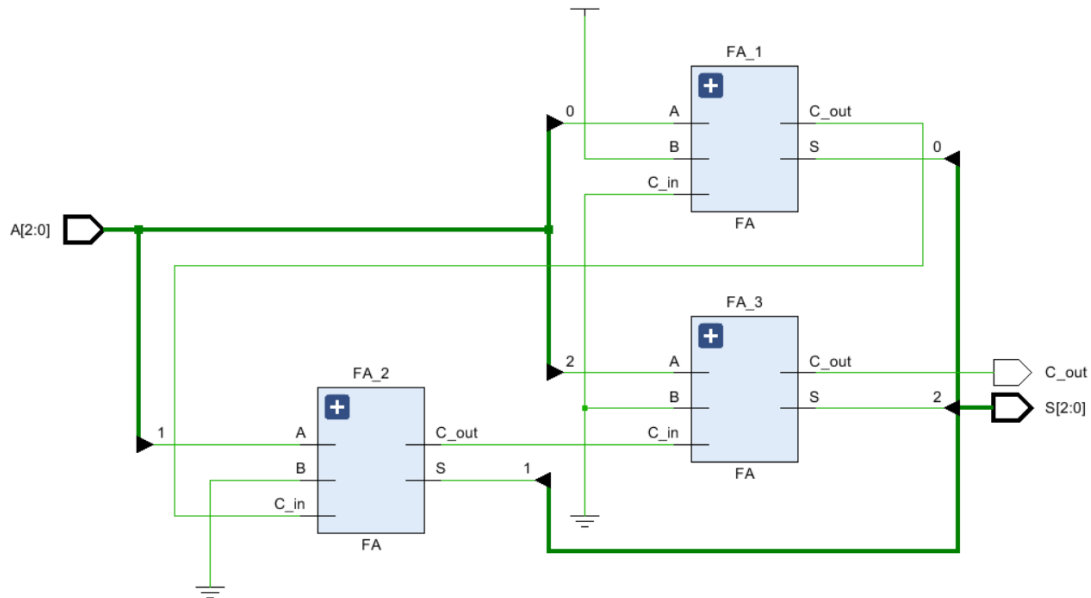

-- Module Name: RCA_3 - Behavioral

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Ripple carry adder that capable of adding 3 bit number
-- Used for incrementing instruction counter signal
entity RCA_3 is
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
          S : out STD_LOGIC_VECTOR (2 downto 0);
          C_out : out STD_LOGIC);
end RCA_3;

architecture Behavioral of RCA_3 is

    -- Full adders used for creating RCA
    component FA
    port (
        A: in std_logic;
        B: in std_logic;
        C_in: in std_logic;
        S: out std_logic;
        C_out: out std_logic);
    end component;

    SIGNAL FA0_S, FA0_C, FA1_S, FA1_C, FA2_S, FA2_C : std_logic;
begin

    FA_1 : FA
    port map (
        A => A(0),
        B => '1', -- Incrementing step

```

```

C_in => '0', -- Set to ground
S => S(0),
C_Out => FA0_C);

FA_2 : FA
port map (
A => A(1),
B => '0',
C_in => FA0_C,
S => S(1),
C_Out => FA1_C);

FA_3 : FA
port map (
A => A(2),
B => '0',
C_in => FA1_C,
S => S(2),
C_Out => C_out);

end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_REG is
-- Port ( );
end TB_REG;

architecture Behavioral of TB_REG is
COMPONENT Reg is
    Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
          En : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (3 downto 0));
end COMPONENT;
COMPONENT Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC);
end COMPONENT;

SIGNAL D : STD_LOGIC_VECTOR (3 downto 0);
SIGNAL En : STD_LOGIC;
SIGNAL Clk_in, Clk_out : STD_LOGIC;
SIGNAL Q : STD_LOGIC_VECTOR (3 downto 0);
begin
UUT:Reg PORT MAP(D,En,Clk_out,Q);
UUT1:Slow_Clk PORT MAP(Clk_in,Clk_out);
PROCESS BEGIN
Clk_in<='1';
wait for 3 ns;
Clk_in<='0';
wait for 3 ns;

```

```


end process;
process begin
D<="1001";
En<='1';
wait for 100 ns;
En<='0';
wait for 100 ns;
D<="1111";
En<='1';
wait for 100 ns;
En<='0';
END PROCESS;

```

end Behavioral;

Name	Value	0 ns	100 ns	200 ns	300 ns	400 ns	500 ns	600 ns	700 ns	800 ns
> A[2:0]	000	000	001	010	011	100	101	110	111	010
> S[2:0]	001	001	010	011	100	101	110	111	000	011
C_out	0									

- Program Counter

 

-- Module Name: Program_Counter - Behavioral

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

-- Instruction counter.
-- Press Reset button to start from 000 instruction.
-- Output Mux or normal counting accordingly
-- Synchronized by a slow clock
entity Program_Counter is
    Port ( Reset : in STD_LOGIC;
          Clk : in std_logic;
          M_in : in STD_LOGIC_VECTOR (2 downto 0);
          M_Sel : out STD_LOGIC_VECTOR (2 downto 0));
end Program_Counter;

```

```

architecture Behavioral of Program_Counter is
begin
process(Clk, Reset)
begin
    if Reset = '1' then -- check for Reset press
        -- Reset value
        M_Sel<="000";
    elsif rising_edge(Clk) then
        M_Sel<=M_in; -- Update register input from mux output
    end if;
end process;
end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_programcounter is
-- Port ( );
end TB_programcounter;

architecture Behavioral of TB_programcounter is
component Program_Counter is
    Port ( Reset : in STD_LOGIC;
          Clk : in std_logic;
          M_in : in STD_LOGIC_VECTOR (2 downto 0);
          M_Sel : out STD_LOGIC_VECTOR (2 downto 0));
end component;
COMPONENT Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC);
end COMPONENT;

signal Reset:std_logic;
signal M_in,M_Sel : STD_LOGIC_VECTOR (2 downto 0);
SIGNAL Clk_in,Clk_out: STD_LOGIC;
begin

UUT:Program_Counter port map(Reset,Clk_out,M_in,M_Sel);
UUT1:Slow_Clk PORT MAP(Clk_in,Clk_out);
PROCESS BEGIN
Clk_in<='1';
wait for 3 ns;
Clk_in<='0';
wait for 3 ns;
end process;
process begin
Reset<='1';
M_in<="111";
wait for 100 ns;
Reset<='0';
wait for 100 ns;


```

```


M_in<="110";
wait for 100 ns;
M_in<="101";
wait for 100 ns;
M_in<="100";
wait for 100 ns;
M_in<="011";
wait for 100 ns;
M_in<="010";
wait for 100 ns;
M_in<="001";
wait for 100 ns;
M_in<="000";
wait for 100 ns;

end process;
end Behavioral;

```

 

- Instruction Selector

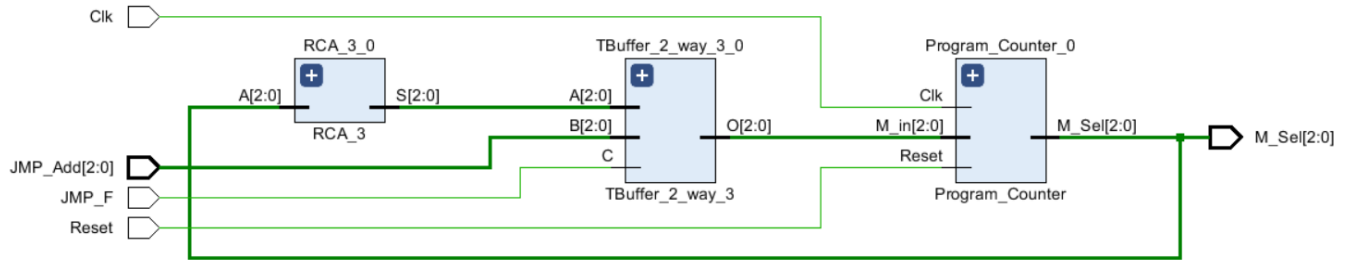

```
-- Module Name: Instruction_Selector - Behavioral
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Instruction_Selector is
```

```
    Port ( Reset : in STD_LOGIC;
```

```
          JMP_F : in STD_LOGIC;
```

```
          JMP_Add : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          Clk : in STD_LOGIC;
```

```
          M_Sel : out STD_LOGIC_VECTOR (2 downto 0));
```

```
end Instruction_Selector;
```

```
architecture Behavioral of Instruction_Selector is
```

```
--Tri state buffer for selecting instructions between jump address and normal counting
```

```
component TBuffer_2_way_3 is
```

```
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          B : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          C : in STD_LOGIC;
```

```
          O : out STD_LOGIC_VECTOR (2 downto 0));
```

```
end component;
```

```
-- Get output and Reset when button pushed
```

```
component Program_Counter is
```

```
    Port ( Reset : in STD_LOGIC;
```

```
          Clk : in std_logic;
```

```
          M_in : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          M_Sel : out STD_LOGIC_VECTOR (2 downto 0));
```

```
end component;
```

```
-- Increment instruction register
```

```
component RCA_3 is
```

```
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          --B : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          S : out STD_LOGIC_VECTOR (2 downto 0);
```

```
          C_out : out STD_LOGIC);
```

```
end component;
```

```
signal mem_out,adder_out,Mux_out:STD_LOGIC_VECTOR (2 downto 0);
```

```

begin
    Program_Counter_0:Program_Counter port map(Reset,Clk,Mux_out,mem_out);
    RCA_3_0:RCA_3 port map(mem_out,adder_out);
    TBuffer_2_way_3_0:TBuffer_2_way_3 port
map(adder_out,JMP_Add,JMP_F,Mux_out);
    M_Sel <= mem_out;
end Behavioral;

```

- Unit testing and Simulation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_PC is
-- Port ( );
end TB_PC;

architecture Behavioral of TB_PC is
component Instruction_Selector is
    Port ( Reset : in STD_LOGIC;
          JMP_F : in STD_LOGIC;
          JMP_Add : in STD_LOGIC_VECTOR (2 downto 0);
          Clk : in STD_LOGIC;
          M_Sel : out STD_LOGIC_VECTOR (2 downto 0));
end component;

component Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC);
end component;

signal Reset : std_logic := '1';
signal JMP_F : STD_LOGIC ;
signal JMP_Add ,M_Sel: STD_LOGIC_VECTOR (2 downto 0);

    signal Clk_in,Clk_out :STD_LOGIC;

begin
    UUT1:Slow_Clk port map(Clk_in,Clk_out);
    UUT2:Instruction_Selector port map(Reset,JMP_F,JMP_Add,Clk_out,M_Sel);

process begin
    Clk_in <= '1';
    wait for 2 ns;
    Clk_in <= '0';
    wait for 2 ns;
end process;

process

begin
    -- Test 1: Reset the program counter
    JMP_F <= '0';
    Reset <= '1';
    wait for 10 ns; -- Give time for the reset to take effect

```




```


Reset <= '0';
wait for 200 ns;
JMP_F <= '0';
wait for 200 ns;
JMP_F <= '0';
wait for 200 ns;
JMP_F <= '0';
wait;
end process;

end Behavioral;

```

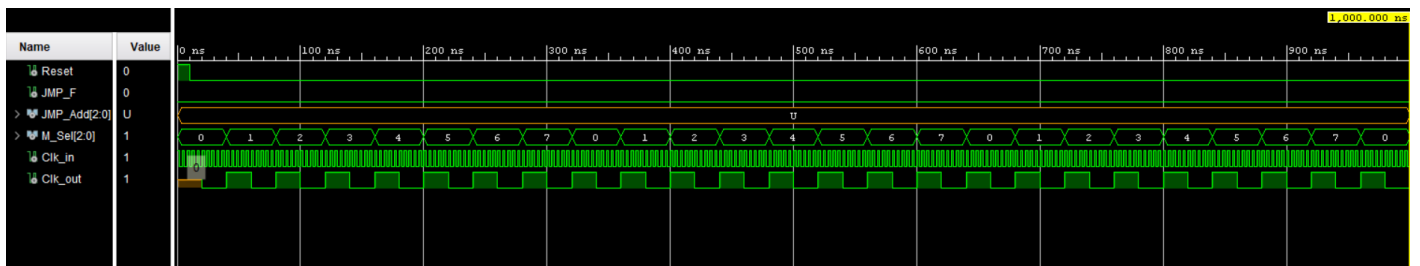

- The Processor

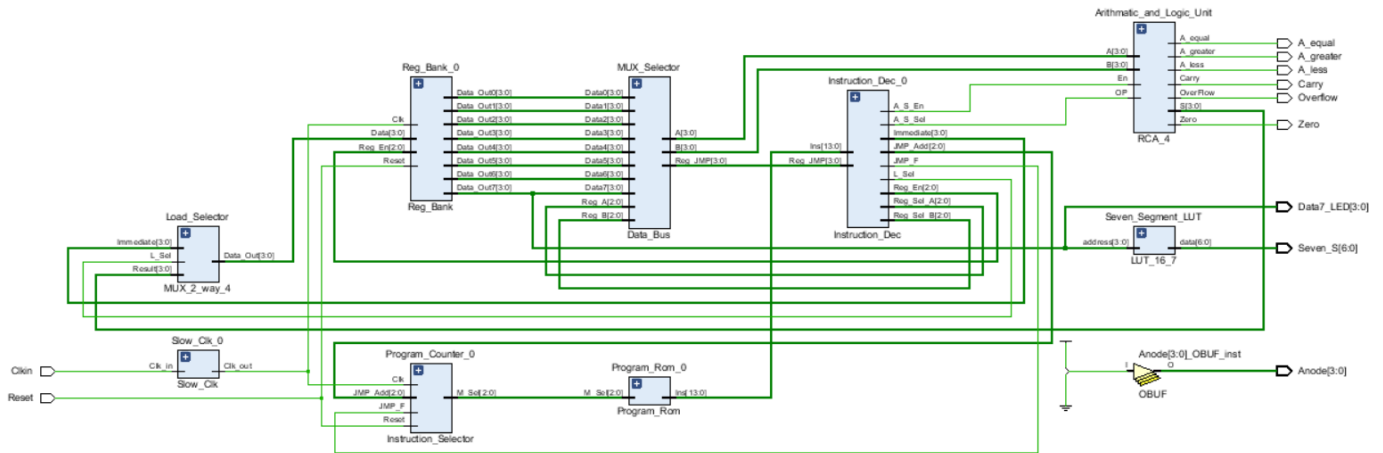

-- Module Name: Processor - Behavioral

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Processor is
    Port ( Clkin : in STD_LOGIC;
          Data7_LED: out std_logic_vector (3 downto 0);
          Overflow ,Zero,Carry,A_less,A_equal,A_greater: out std_logic;
          Reset : in STD_LOGIC;
          Seven_S:out std_logic_vector (6 downto 0);
          Anode : out STD_LOGIC_VECTOR (3 downto 0));
end Processor;

architecture Behavioral of Processor is
    component LUT_16_7 is
        Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
              data : out STD_LOGIC_VECTOR (6 downto 0));
    end component;

    component Instruction_Selector is
        Port ( Reset : in STD_LOGIC;
              JMP_F : in STD_LOGIC;
              JMP_Add : in STD_LOGIC_VECTOR (2 downto 0);
              Clk : in std_logic;
              M_Sel : out STD_LOGIC_VECTOR (2 downto 0));
    end component;

    component Slow_Clk is
        Port ( Clk_in : in STD_LOGIC;
              Clk_out : out STD_LOGIC);
    end component;

    component Instruction_Dec is
        Port ( Ins : in STD_LOGIC_VECTOR (13 downto 0);

```

```

    Reg_JMP : in STD_LOGIC_VECTOR (3 downto 0);
    L_Sel : out STD_LOGIC;
    Immediate : out STD_LOGIC_VECTOR (3 downto 0);
    Reg_Sel_A : out STD_LOGIC_VECTOR (2 downto 0);
    Reg_Sel_B : out STD_LOGIC_VECTOR (2 downto 0);
    A_S_Sel : out STD_LOGIC;
    Reg_En : out STD_LOGIC_VECTOR (2 downto 0);
    JMP_F : out STD_LOGIC;
    JMP_Add : out STD_LOGIC_VECTOR (2 downto 0);
    A_S_En:out std_logic);
end component;
component Program_Rom is
    Port ( --Reg_Ins:in STD_LOGIC_VECTOR (11 downto 0);
        M_Sel : in STD_LOGIC_VECTOR (2 downto 0);
        Ins : out STD_LOGIC_VECTOR (13 downto 0));
end component;
component MUX_2_way_4 is
    Port ( Immediate : in STD_LOGIC_VECTOR (3 downto 0);
        Result : in STD_LOGIC_VECTOR (3 downto 0);
        L_Sel : in STD_LOGIC;
        Data_Out : out STD_LOGIC_VECTOR (3 downto 0));
end component;
component Reg_Bank is
    Port ( Clk : in STD_LOGIC;
        Reset : in STD_LOGIC;
        Reg_En : in STD_LOGIC_VECTOR (2 downto 0);
        Data : in STD_LOGIC_VECTOR (3 downto 0);
        Data_Out0 : out STD_LOGIC_VECTOR (3 downto 0);
        Data_Out1 : out STD_LOGIC_VECTOR (3 downto 0);
        Data_Out2 : out STD_LOGIC_VECTOR (3 downto 0);
        Data_Out3 : out STD_LOGIC_VECTOR (3 downto 0);
        Data_Out4 : out STD_LOGIC_VECTOR (3 downto 0);
        Data_Out5 : out STD_LOGIC_VECTOR (3 downto 0);
        Data_Out6 : out STD_LOGIC_VECTOR (3 downto 0);
        Data_Out7 : out STD_LOGIC_VECTOR (3 downto 0));
end component;
component Data_Bus is
    Port ( Data0 : in STD_LOGIC_VECTOR (3 downto 0);
        Data1 : in STD_LOGIC_VECTOR (3 downto 0);
        Data2 : in STD_LOGIC_VECTOR (3 downto 0);
        Data3 : in STD_LOGIC_VECTOR (3 downto 0);
        Data4 : in STD_LOGIC_VECTOR (3 downto 0);
        Data5 : in STD_LOGIC_VECTOR (3 downto 0);
        Data6 : in STD_LOGIC_VECTOR (3 downto 0);
        Data7 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg_A : in STD_LOGIC_VECTOR (2 downto 0);
        Reg_B : in STD_LOGIC_VECTOR (2 downto 0);
        Reg_JMP : out STD_LOGIC_vector (3 downto 0);
        A : out STD_LOGIC_VECTOR (3 downto 0);
        B : out STD_LOGIC_VECTOR (3 downto 0));
end component;
component RCA_4 is
    Port (
        A: in STD_LOGIC_VECTOR (3 downto 0) ;
        B:in STD_LOGIC_VECTOR (3 downto 0);
        OP,En : in STD_LOGIC;
        S : out STD_LOGIC_VECTOR (3 downto 0);

```

```

        Overflow,Zero,Carry,A_less,A_equal,A_greater : out STD_LOGIC);
end component;

signal JMP_f,L_Sel,A_S_Sel,Clk,vA_S_En:std_logic;

signal A,B,Reg_check_JMP ,Immediate,Result,Data_Reg
,Reg_Data_Out0,Reg_Data_Out1,Reg_Data_Out2,Reg_Data_Out3,Reg_Data_Out4,Reg_Data_Out5,Reg_Data_Out6,Reg_Data_Out7 :std_logic_vector(3 downto 0);

signal JMPadd,msel,Reg_Sel_A,Reg_Sel_B,Reg_En :std_logic_vector(2 downto 0);

signal insts :std_logic_vector(13 downto 0);

begin
-- Program counter mapping
    Program_Counter_0:Instruction_Selector port
map(Reset,JMP_f,JMPadd,Clk,msel);

-- Program Rom mapping
    Program_Rom_0:Program_Rom port map(msel,insts);

-- Instruction Decoder mapping
    Instruction_Dec_0:Instruction_Dec port
map(insts,Reg_check_JMP,L_Sel,Immediate,Reg_Sel_A,Reg_Sel_B,A_S_Sel,Reg_En,JMP_f,JMPadd,vA_S_En);

-- Load selector mapping
    Load_Selector:MUX_2_way_4 port map(Immediate,Result,L_Sel,Data_Reg);

-- Reg Bank mapping
    Reg_Bank_0:Reg_Bank port
map(Clk,Reset,Reg_En,Data_Reg,Reg_Data_Out0,Reg_Data_Out1,Reg_Data_Out2,Reg_Data_Out3,Reg_Data_Out4,Reg_Data_Out5,Reg_Data_Out6,Reg_Data_Out7);

-- MUX Selector mapping
    MUX_Selector:Data_Bus port
map(Reg_Data_Out0,Reg_Data_Out1,Reg_Data_Out2,Reg_Data_Out3,Reg_Data_Out4,Reg_Data_Out5,Reg_Data_Out6,Reg_Data_Out7,Reg_Sel_A,Reg_Sel_B,Reg_check_JMP,A,B);

-- ALU mapping
    Arithmetic_and_Logic_Unit:RCA_4 port
map(A,B,A_S_Sel,vA_S_En,Result,Overflow,Zero,Carry,A_less,A_equal,A_greater);

-- Slow Clock
    Slow_Clk_0:Slow_Clk port map(Clkin,Clk);

-- Seven segment lookup table
    Seven_Segment_LUT:LUT_16_7 port map(Reg_Data_Out7,Seven_S);

-- Led Output R7 register
Data7_LED<=Reg_Data_Out7;

-- Anode for seven segment
Anode <= "1110";

```

```
end Behavioral;
```

- System testing and Simulation

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity TB_nano is
-- Port ( );
end TB_nano;

architecture Behavioral of TB_nano is

component Processor is
    Port ( Clkin : in STD_LOGIC;
          Data7_LED: out std_logic_vector (3 downto 0);
          Overflow ,Zero,Carry,A_less,A_equal,A_greater: out std_logic;
          Reset : in STD_LOGIC;
          Seven_S:out std_logic_vector (6 downto 0);
          Anode : out STD_LOGIC_VECTOR (3 downto 0);
          M_Sel : out STD_LOGIC_VECTOR (2 downto 0);
          Clk_out : out STD_LOGIC;
          L_Sel : out STD_LOGIC;
          Immediate : out STD_LOGIC_VECTOR (3 downto 0);
          Reg_Sel_A : out STD_LOGIC_VECTOR (2 downto 0);
          Reg_Sel_B : out STD_LOGIC_VECTOR (2 downto 0);
          A_S_Sel : out STD_LOGIC;
          Reg_En : out STD_LOGIC_VECTOR (2 downto 0);
          JMP_F : out STD_LOGIC;
          JMP_Add : out STD_LOGIC_VECTOR (2 downto 0);
          Ins : out STD_LOGIC_VECTOR (13 downto 0);
          Data_Out : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out0 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out1 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out2 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out3 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out4 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out5 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out6 : out STD_LOGIC_VECTOR (3 downto 0);
          Data_Out7 : out STD_LOGIC_VECTOR (3 downto 0);
          Reg_JMP : out STD_LOGIC_vector (3 downto 0);
          A : out STD_LOGIC_VECTOR (3 downto 0);
          B : out STD_LOGIC_VECTOR (3 downto 0)
    );
end component;

signal Clkin : STD_LOGIC;
signal Data7_LED: std_logic_vector (3 downto 0);
signal Overflow ,Zero,Carry,A_less,A_equal,A_greater:std_logic;
signal Reset : STD_LOGIC;
signal Seven_S: std_logic_vector (6 downto 0);
signal Anode : STD_LOGIC_VECTOR (3 downto 0);

signal M_Sel : STD_LOGIC_VECTOR (2 downto 0);
signal Clk_out : STD_LOGIC;
```

```


signal L_Sel : STD_LOGIC;
signal Immediate : STD_LOGIC_VECTOR (3 downto 0);
signal Reg_Sel_A : STD_LOGIC_VECTOR (2 downto 0);
signal Reg_Sel_B : STD_LOGIC_VECTOR (2 downto 0);
signal A_S_Sel : STD_LOGIC;
signal Reg_En : STD_LOGIC_VECTOR (2 downto 0);
signal JMP_F : STD_LOGIC;
signal JMP_Add : STD_LOGIC_VECTOR (2 downto 0);
signal Ins : STD_LOGIC_VECTOR (13 downto 0);
signal Data_Out : STD_LOGIC_VECTOR (3 downto 0);
signal Data_Out0 : STD_LOGIC_VECTOR (3 downto 0);
signal Data_Out1 : STD_LOGIC_VECTOR (3 downto 0);
signal Data_Out2 : STD_LOGIC_VECTOR (3 downto 0);
signal Data_Out3 : STD_LOGIC_VECTOR (3 downto 0);
signal Data_Out4 : STD_LOGIC_VECTOR (3 downto 0);
signal Data_Out5 : STD_LOGIC_VECTOR (3 downto 0);
signal Data_Out6 : STD_LOGIC_VECTOR (3 downto 0);
signal Data_Out7 : STD_LOGIC_VECTOR (3 downto 0);
signal Reg_JMP : STD_LOGIC_vector (3 downto 0);
signal A : STD_LOGIC_VECTOR (3 downto 0);
signal B : STD_LOGIC_VECTOR (3 downto 0);

begin
    UUT:Processor port map(Clkin,Data7_LED,Overflow
    ,Zero,Carry,A_less,A_equal,A_greater,Reset,Seven_S,Anode,M_Sel,Clk_out,L_Sel,
    Immediate,Reg_Sel_A,Reg_Sel_B,A_S_Sel,Reg_En,JMP_F,JMP_Add,Ins,Data_Out,Data_
    Out0,Data_Out1,Data_Out2,Data_Out3,Data_Out4,Data_Out5,
    Data_Out6,Data_Out7,Reg_JMP,A,B);

    process begin
        Clkin<='1';
        wait for 3 ns;
        Clkin<='0';
        wait for 3 ns;
    end process;
    process begin
        Reset<='1';
        wait for 100 ns;
        Reset<='0';
        wait;
    end process;

end Behavioral;

```

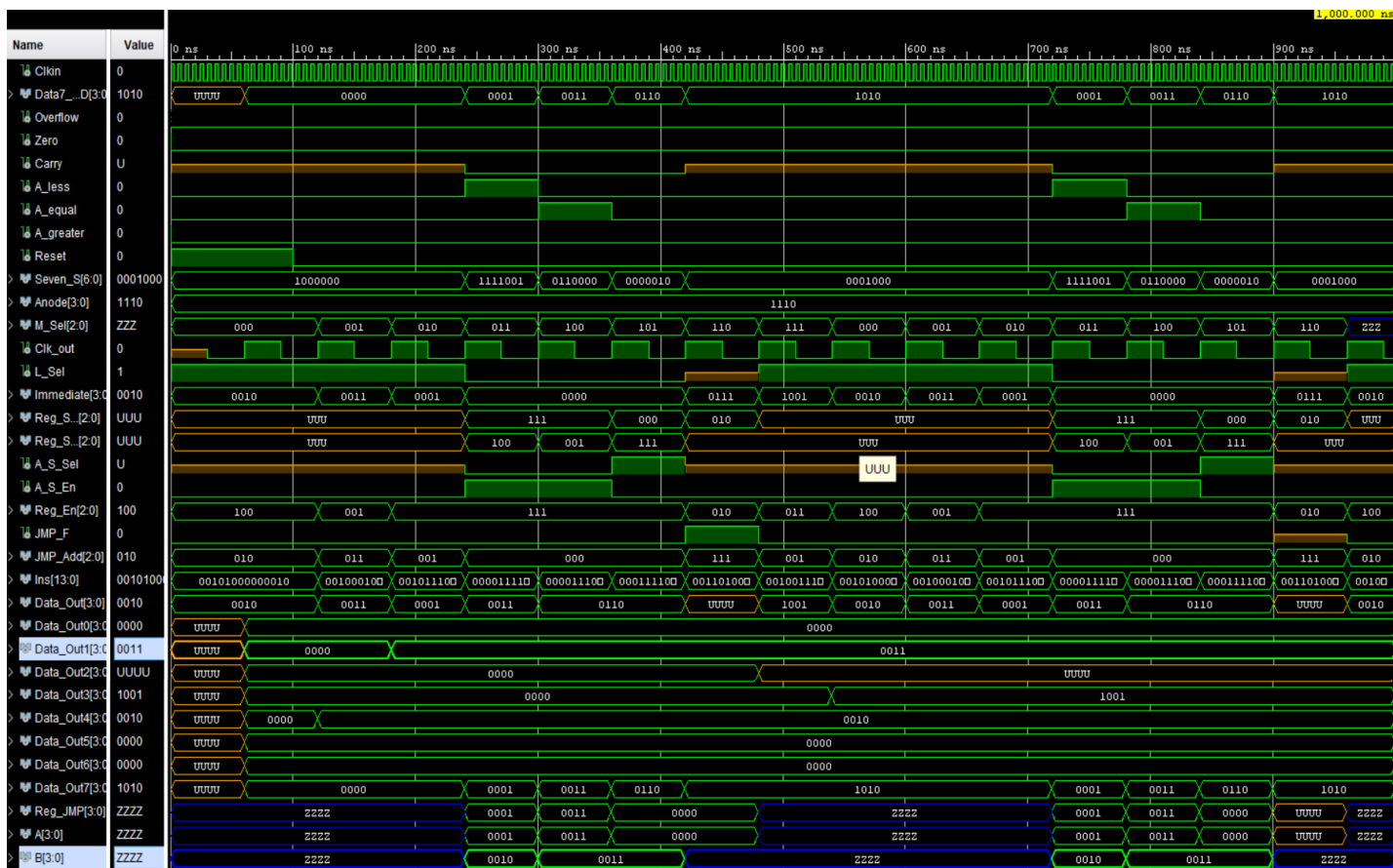

Constraint File

```
1  ## Clock signal
2  set_property PACKAGE_PIN W5 [get_ports Clkin]
3      set_property IOSTANDARD LVCMOS33 [get_ports Clkin]
4      create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports Clkin]
5
6  ## LEDs
7  set_property PACKAGE_PIN U16 [get_ports {Data7_LED[0]}]
8      set_property IOSTANDARD LVCMOS33 [get_ports {Data7_LED[0]}]
9  set_property PACKAGE_PIN E19 [get_ports {Data7_LED[1]}]
10     set_property IOSTANDARD LVCMOS33 [get_ports {Data7_LED[1]}]
11 set_property PACKAGE_PIN U19 [get_ports {Data7_LED[2]}]
12     set_property IOSTANDARD LVCMOS33 [get_ports {Data7_LED[2]}]
13 set_property PACKAGE_PIN V19 [get_ports {Data7_LED[3]}]
14     set_property IOSTANDARD LVCMOS33 [get_ports {Data7_LED[3]}]
15
16 set_property PACKAGE_PIN W3 [get_ports {A_greater}]
17     set_property IOSTANDARD LVCMOS33 [get_ports {A_greater}]
18 set_property PACKAGE_PIN U3 [get_ports {A_equal}]
19     set_property IOSTANDARD LVCMOS33 [get_ports {A_equal}]
20 set_property PACKAGE_PIN P3 [get_ports {A_less}]
21     set_property IOSTANDARD LVCMOS33 [get_ports {A_less}]
22 set_property PACKAGE_PIN N3 [get_ports {Overflow}]
23     set_property IOSTANDARD LVCMOS33 [get_ports {Overflow}]
24 set_property PACKAGE_PIN P1 [get_ports {Zero}]
25     set_property IOSTANDARD LVCMOS33 [get_ports {Zero}]
26 set_property PACKAGE_PIN L1 [get_ports {Carry}]
27     set_property IOSTANDARD LVCMOS33 [get_ports {Carry}]
28
29
30 ##7 segment display
31 set_property PACKAGE_PIN W7 [get_ports {Seven_S[0]}]
32     set_property IOSTANDARD LVCMOS33 [get_ports {Seven_S[0]}]
33 set_property PACKAGE_PIN W6 [get_ports {Seven_S[1]}]
34     set_property IOSTANDARD LVCMOS33 [get_ports {Seven_S[1]}]
35 set_property PACKAGE_PIN U8 [get_ports {Seven_S[2]}]
36     set_property IOSTANDARD LVCMOS33 [get_ports {Seven_S[2]}]
37 set_property PACKAGE_PIN V8 [get_ports {Seven_S[3]}]
38     set_property IOSTANDARD LVCMOS33 [get_ports {Seven_S[3]}]
39 set_property PACKAGE_PIN U5 [get_ports {Seven_S[4]}]
40     set_property IOSTANDARD LVCMOS33 [get_ports {Seven_S[4]}]
41 set_property PACKAGE_PIN V5 [get_ports {Seven_S[5]}]
42     set_property IOSTANDARD LVCMOS33 [get_ports {Seven_S[5]}]
43 set_property PACKAGE_PIN U7 [get_ports {Seven_S[6]}]
44     set_property IOSTANDARD LVCMOS33 [get_ports {Seven_S[6]}]
45
46
47 set_property PACKAGE_PIN U2 [get_ports {Anode[0]}]
48     set_property IOSTANDARD LVCMOS33 [get_ports {Anode[0]}]
49 set_property PACKAGE_PIN U4 [get_ports {Anode[1]}]
50     set_property IOSTANDARD LVCMOS33 [get_ports {Anode[1]}]
51 set_property PACKAGE_PIN V4 [get_ports {Anode[2]}]
52     set_property IOSTANDARD LVCMOS33 [get_ports {Anode[2]}]
53 set_property PACKAGE_PIN W4 [get_ports {Anode[3]}]
54     set_property IOSTANDARD LVCMOS33 [get_ports {Anode[3]}]
55
56
57 ##Buttons
58 set_property PACKAGE_PIN U18 [get_ports Reset]
59     set_property IOSTANDARD LVCMOS33 [get_ports Reset]
60
```


Strategies used to optimize resource consumption

To optimize resource consumption in our Nano processor design, we employed several key strategies:

1. **Avoidance of Lookup Tables for Instruction Decode** - Instead of using lookup tables (LUTs) for instruction decoding, we implemented the instruction decoder using basic logic gates (AND, NOT, NOR, OR, XNOR). This approach significantly reduced the area and power consumption of the instruction decoding circuitry.
2. **Utilization of Tristate Buffers Over Multiplexers** - In our design, we chose to use tristate buffers for data selection instead of multiplexers. Tristate buffers helped simplify the circuitry and contributed to better resource utilization.
3. **Optimized VHDL Implementation** - When implementing the instruction decoder in VHDL, we avoided using if-else or case statements. Instead, we directly used logic gates, which allowed the synthesis tool to optimize the logic more efficiently. This approach resulted in a more compact and optimized hardware implementation.

These strategies were chosen to reduce the complexity of our Nano processor design, leading to a more efficient use of resources such as logic elements and power. By optimizing these aspects of our design, we aimed to create a Nano processor that delivers high performance while minimizing resource consumption.

Resource utilization report

Copyright 1986-2018 Xilinx, Inc. All Rights Reserved.

```
-----
| Tool Version : Vivado v.2018.2.1 (win64) Build 2288692 Thu Jul 26 18:24:02
MDT 2018
| Date       : Sun May  5 01:24:29 2024
| Host      : DESKTOP-3045960 running 64-bit major release (build 9200)
| Command   : report_utilization -file {C:/Users/DASUN/Downloads/Telegram
Desktop/latest update.xpr/utilization.txt} -name utilization_1
| Design    : Processor
| Device    : 7a35tcpg236-1
| Design State : Routed
-----
```

Utilization Design Information

Table of Contents

- ```

1. Slice Logic
1.1 Summary of Registers by Type
2. Slice Logic Distribution
3. Memory
4. DSP
5. IO and GT Specific
6. Clocking
7. Specific Feature
8. Primitives
9. Black Boxes
10. Instantiated Netlists
```

#### 1. Slice Logic

```

+-----+-----+-----+-----+-----+
| Site Type | Used | Fixed | Available | Util% |
+-----+-----+-----+-----+-----+
Slice LUTs	117	0	20800	0.56
LUT as Logic	117	0	20800	0.56
LUT as Memory	0	0	9600	0.00
Slice Registers	57	0	41600	0.14
Register as Flip Flop	57	0	41600	0.14
Register as Latch	0	0	41600	0.00
F7 Muxes	0	0	16300	0.00
F8 Muxes	0	0	8150	0.00
+-----+-----+-----+-----+-----+
```

#### 1.1 Summary of Registers by Type

```

+-----+-----+-----+-----+-----+
```

| Total | Clock Enable | Synchronous | Asynchronous |
|-------|--------------|-------------|--------------|
| 0     | -            | -           | -            |
| 0     | -            | -           | Set          |
| 0     | -            | -           | Reset        |
| 0     | -            | Set         | -            |
| 0     | -            | Reset       | -            |
| 0     | Yes          | -           | -            |
| 0     | Yes          | -           | Set          |
| 3     | Yes          | -           | Reset        |
| 0     | Yes          | Set         | -            |
| 54    | Yes          | Reset       | -            |

## 2. Slice Logic Distribution

| Util% | Site Type                               | Used | Fixed | Available |
|-------|-----------------------------------------|------|-------|-----------|
| 0.58  | Slice                                   | 47   | 0     | 8150      |
|       | SLICEL                                  | 35   | 0     |           |
|       | SLICEM                                  | 12   | 0     |           |
| 0.56  | LUT as Logic                            | 117  | 0     | 20800     |
|       | using O5 output only                    | 0    |       |           |
|       | using O6 output only                    | 76   |       |           |
|       | using O5 and O6                         | 41   |       |           |
| 0.00  | LUT as Memory                           | 0    | 0     | 9600      |
|       | LUT as Distributed RAM                  | 0    | 0     |           |
|       | LUT as Shift Register                   | 0    | 0     |           |
| 0.04  | LUT Flip Flop Pairs                     | 8    | 0     | 20800     |
|       | fully used LUT-FF pairs                 | 0    |       |           |
|       | LUT-FF pairs with one unused LUT output | 5    |       |           |
|       | LUT-FF pairs with one unused Flip Flop  | 8    |       |           |
|       | Unique Control Sets                     | 6    |       |           |

\* Note: Review the Control Sets Report for more information regarding control sets.

### 3. Memory

-----

| Site Type      | Used | Fixed | Available | Util% |
|----------------|------|-------|-----------|-------|
| Block RAM Tile | 0    | 0     | 50        | 0.00  |
| RAMB36/FIFO*   | 0    | 0     | 50        | 0.00  |
| RAMB18         | 0    | 0     | 100       | 0.00  |

\* Note: Each Block RAM Tile only has one FIFO logic available and therefore can accommodate only one FIFO36E1 or one FIFO18E1. However, if a FIFO18E1 occupies a Block RAM Tile, that tile can still accommodate a RAMB18E1

### 4. DSP

-----

| Site Type | Used | Fixed | Available | Util% |
|-----------|------|-------|-----------|-------|
| DSPs      | 0    | 0     | 90        | 0.00  |

### 5. IO and GT Specific

-----

| Site Type                   | Used | Fixed | Available | Util% |
|-----------------------------|------|-------|-----------|-------|
| Bonded IOB                  | 23   | 23    | 106       | 21.70 |
| IOB Master Pads             | 9    |       |           |       |
| IOB Slave Pads              | 14   |       |           |       |
| Bonded IPADs                | 0    | 0     | 10        | 0.00  |
| Bonded OPADs                | 0    | 0     | 4         | 0.00  |
| PHY_CONTROL                 | 0    | 0     | 5         | 0.00  |
| PHASER_REF                  | 0    | 0     | 5         | 0.00  |
| OUT_FIFO                    | 0    | 0     | 20        | 0.00  |
| IN_FIFO                     | 0    | 0     | 20        | 0.00  |
| IDELAYCTRL                  | 0    | 0     | 5         | 0.00  |
| IBUFDS                      | 0    | 0     | 104       | 0.00  |
| GTPE2_CHANNEL               | 0    | 0     | 2         | 0.00  |
| PHASER_OUT/PHASER_OUT_PHY   | 0    | 0     | 20        | 0.00  |
| PHASER_IN/PHASER_IN_PHY     | 0    | 0     | 20        | 0.00  |
| IDELAYE2/IDELAYE2_FINEDELAY | 0    | 0     | 250       | 0.00  |
| IBUFDS_GTE2                 | 0    | 0     | 2         | 0.00  |
| ILOGIC                      | 0    | 0     | 106       | 0.00  |
| OLOGIC                      | 0    | 0     | 106       | 0.00  |

### 6. Clocking

-----

| Site Type  | Used | Fixed | Available | Util% |
|------------|------|-------|-----------|-------|
| BUFGCTRL   | 1    | 0     | 32        | 3.13  |
| BUFIO      | 0    | 0     | 20        | 0.00  |
| MMCME2_ADV | 0    | 0     | 5         | 0.00  |
| PLLE2_ADV  | 0    | 0     | 5         | 0.00  |
| BUFMRCE    | 0    | 0     | 10        | 0.00  |
| BUFHCE     | 0    | 0     | 72        | 0.00  |
| BUFR       | 0    | 0     | 20        | 0.00  |

## 7. Specific Feature

-----

| Site Type   | Used | Fixed | Available | Util% |
|-------------|------|-------|-----------|-------|
| BSCANE2     | 0    | 0     | 4         | 0.00  |
| CAPTUREE2   | 0    | 0     | 1         | 0.00  |
| DNA_PORT    | 0    | 0     | 1         | 0.00  |
| EFUSE_USR   | 0    | 0     | 1         | 0.00  |
| FRAME_ECCE2 | 0    | 0     | 1         | 0.00  |
| ICAPE2      | 0    | 0     | 2         | 0.00  |
| PCIE_2_1    | 0    | 0     | 1         | 0.00  |
| STARTUPE2   | 0    | 0     | 1         | 0.00  |
| XADC        | 0    | 0     | 1         | 0.00  |

## 8. Primitives

-----

| Ref Name | Used | Functional Category |
|----------|------|---------------------|
| LUT2     | 71   | LUT                 |
| FDRE     | 54   | Flop & Latch        |
| LUT4     | 47   | LUT                 |
| OBUF     | 21   | IO                  |
| LUT3     | 15   | LUT                 |
| LUT6     | 13   | LUT                 |
| LUT5     | 11   | LUT                 |
| CARRY4   | 8    | CarryLogic          |
| FDCE     | 3    | Flop & Latch        |
| IBUF     | 2    | IO                  |
| LUT1     | 1    | LUT                 |
| BUFG     | 1    | Clock               |

## 9. Black Boxes

-----

| Ref Name | Used |  |
|----------|------|--|

## 10. Instantiated Netlists

| Ref Name | Used |  |
|----------|------|--|

## **Implemented additional features**

In our Nano processor design, we extended the given 12-bit instructions to 14-bit instructions to incorporate additional commands, namely SUB, NOP, and JMP, expanding the functionality of the processor.

1. Sub Command - For the SUB command, we added the opcode 0100 to the instructions and introduced new signals from the instruction decoder to the multiplexer selector to be used with the subtractor. The subtractor is a crucial component for subtracting values, as it first converts the second number to its two's complement and then adds it to the first number.
2. NOP Command - The nop command was implemented by adding logic to the instruction decoder and the opcode is 0101. This command effectively does nothing but pass the clock cycle, providing a way to introduce delays or synchronize operations.
3. JMP Command - Inspired by the JZR opcode, we implemented the jmp command to jump to a specific instruction in the program. This command is particularly useful for creating loop structures within programs, enhancing the flexibility and control flow of the processor.
4. Comparator Unit - We also added a comparator unit to the adder/subtractor unit, extending its functionality. The comparator unit includes additional LEDs to indicate whether the first value is greater, equal, or lower than the second value. This feature is especially useful for comparing values in the registers and is capable of handling both positive and negative numbers within the range of -8 to 7, given the 4-bit representation of numbers in our design.

By adding these additional features, we have enhanced the functionality and versatility of our Nano processor, providing more capabilities for executing a wider range of instructions and operations. Additionally, by extending the instruction set to 14 bits, we have ensured that the processor is easily scalable and can accommodate further enhancements and modifications in the future.

### **Individual contributions**

(01) Illangasinghe I.M.D.P

- Designed and developed

|                          | Deign time | Develop time |
|--------------------------|------------|--------------|
| Program rom              | 30min      | 4h           |
| Instruction decoder      | 2h         | 10h          |
| Program counter          | 1h         | 3h           |
| Instruction selector     | 30min      | 30min        |
| 3-bit ripple carry adder | 30min      | 30min        |
| 2-way 3-bit multiplexer  | 30min      | 30min        |
| 2-way 4-bit multiplexer  | 30min      | 30min        |
| 4-bit Adder /subtractor  | 2h         | 3h           |
| Comparator unit          | 1h         | 30min        |
| Register bank            | 30min      | 30min        |
| Mux selector             | 30min      | 2h           |

- Simulation and testing

Testbenches - 2h

4-bit Register

Register bank

ALU & Comparator

Decoder 3 to 8

Decoder 2 to 4

MUX selector

Seven Segment lookup table

3-bit Ripple carry adder

Program rom



(02) Dissanayake D.M.S.H

- Designed and developed

|                             | Deign time | Develop time |
|-----------------------------|------------|--------------|
| Tri State Buffer            | 15min      | 30min        |
| Tri State Buffer (Inverted) | 15min      | 20min        |
| Optimized 2-way 4-bit Mux   | 30min      | --           |
| 8-way 4-bit multiplexer     | 1h         | 1h           |
| Mux Selector                | --         | 1h           |
| 2 to 4 Decoder 4-bit        | 30min      | 30min        |
| 3 to 8 Decoder 4-bit        | 30min      | 30min        |
| Instruction Decoder         | --         | 2h           |

- Simulation and testing

Testbenches - 1h

Tri State Buffer

Tri State Buffer (Inverted)

2-way 4-bit Mux

8-way 4-bit multiplexer

2 to 4 Decoder 4 bit

3 to 8 Decoder 4 bit

- Creating the constraint file and mapping the outputs - 30min
- Assembling the design diagrams, VHDL codes and simulations and creating the lab report – 6h

(03) Balasuriya B.D.S.K

- Designed and developed

|                               | Design time | Develop time |
|-------------------------------|-------------|--------------|
| 4-bit Add/Subtract unit       | 30min       | 30min        |
| 3-bit adder                   | 20min       | 20min        |
| 3-bit Program Counter (PC)    | 40min       | 1h           |
| k-way b-bit multiplexers      | 2h          | 1h           |
| k-way b-bit Tri-state buffers | 2h          | 1h           |
| Register Bank                 | 1h          | 30min        |
| Program ROM                   | 30min       | 30min        |
| Instruction Decoder           | --          | 2h           |

- Simulation and testing

Testbenches - 2h

4-bit Add/Subtract unit

3-bit adder

3-bit Program Counter (PC)

k-way b-bit multiplexers

k-way b-bit Tri-state buffers

Register Bank

Program ROM

(04) Fernando K.M.I

- Designed and developed

|                               | Design time | Develop time |
|-------------------------------|-------------|--------------|
| 4-bit Add/Subtract unit       | 30min       | 30min        |
| 3-bit adder                   | 20min       | 20min        |
| 3-bit Program Counter (PC)    | 40min       | 1h           |
| k-way b-bit multiplexers      | 2h          | 1h           |
| k-way b-bit Tri-state buffers | 2h          | 1h           |
| Register Bank                 | 1h          | 30min        |
| Program ROM                   | 30min       | 30min        |
| Instruction Decoder           | --          | 2h           |

- Simulation and testing

Testbenches - 2h

4-bit Add/Subtract unit

3-bit adder

3-bit Program Counter (PC)

k-way b-bit multiplexers

k-way b-bit Tri-state buffers

Register Bank

Program ROM

- The testing on Basys 3 board was done by all the team members - 5h

***CS1050 - Computer Organization and Digital Design***

***Nanoprocessor Design Competition***

**Group number – 14**

*Members:*

| <i>Name</i>           | <i>Index number</i> |
|-----------------------|---------------------|
| Illangasinghe I.M.D.P | 220234R             |
| Dissanayake D.M.S.H   | 220138C             |
| Balasuriya B.D.S.K    | 220056X             |
| Fernando K.M.I        | 220166J             |